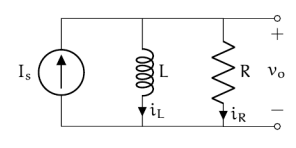


can.exe Exercises for Chapter can

Exercise can.mod

Use the diagram below to answer the following questions and imperatives. Let $I_s = A_0$, where $A_0 \in \mathbb{R}$ is a known constant. Perform a full circuit analysis, including the transient response. The initial inductor current is $i_L(0) = 0$.


- Write the elemental, KCL, and KVL equations.
- Write the differential equation for $i_L(t)$ arranged in the standard form and identify the time constant τ .
- Solve the differential equation for $i_L(t)$ and use the solution to find the output voltage $v_o(t)$.



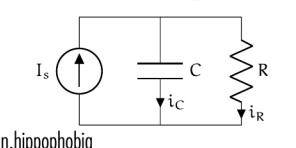Exercise can.theoretically


Use the diagram below to answer the following questions and imperatives. Let $I_s = A_0$, where $A_0 \in \mathbb{R}$ is a known constant. Perform a full circuit analysis, including the transient response. The initial capacitor voltage is $v_C(0) = v_{C0}$, a known constant.

- Write the elemental, KCL, and KVL equations.
- Write the differential equation for $v_C(t)$ arranged in the standard form.
- Solve the differential equation for $v_C(t)$.



Exercise can.hippohoto

For the RC circuit diagram below, perform a complete circuit analysis to solve for $v_o(t)$ if $V_s(t) = A \sin \omega t$, where $A \in \mathbb{R}$ is a given amplitude and $\omega \in \mathbb{R}$ is a given angular frequency. Let $i_L(t)|_{t=0} = 0$ be the initial inductor current. Hint: you will need to solve a differential equation for $v_C(t)$.

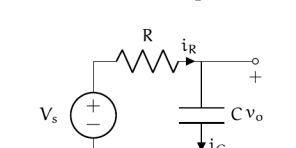


Elemental Eq's
 $V_R = i_R R$ $V_C = V_s$
 $\frac{dV_C}{dt} = \frac{1}{C} i_C$ $V_s = A \sin \omega t$
 KCL $i_R = i_C$
 KVL $V_s = V_R + V_C$

$\frac{dV_C}{dt} = \frac{1}{C} i_C = \frac{1}{RC} (V_s - V_C)$
 $\frac{dV_C}{dt} + \frac{1}{RC} V_C = \frac{1}{RC} A \sin(\omega t)$

Exercise can.frustration


For the circuit diagram below, perform a complete circuit analysis to solve for $v_o(t)$ if $V_s(t) = A \sin \omega t$, where $A \in \mathbb{R}$ is a given amplitude and $\omega \in \mathbb{R}$ is a given angular frequency. Let $i_L(t)|_{t=0} = 0$ be the initial inductor current. Hint: you will need to solve a differential equation for $i_L(t)$.

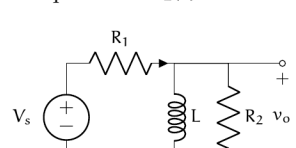

$\lambda + \frac{1}{RC} = 0 \Rightarrow \lambda = -\frac{1}{RC}$
 $V_C = C_1 e^{-t/RC}$
 $V_C = K_1 \sin(\omega t) + K_2 \cos(\omega t)$
 $\frac{dV_C}{dt} = K_1 \omega \cos(\omega t) - K_2 \omega \sin(\omega t)$
 $K_1 \omega \cos(\omega t) - K_2 \omega \sin(\omega t) + \frac{1}{RC} (K_1 \sin(\omega t) + K_2 \cos(\omega t)) = \frac{A \sin(\omega t)}{RC}$
 $K_1 \omega \cos(\omega t) - K_2 \omega \sin(\omega t) + \frac{K_1}{RC} \sin(\omega t) + \frac{K_2}{RC} \cos(\omega t) = 0$
 $-K_1 \omega + \frac{K_2}{RC} = 0 \Rightarrow K_1 \omega = \frac{K_2}{RC}$
 $V_C = C_1 e^{-t/RC} + K_1 \sin(\omega t) + K_2 \cos(\omega t)$
 $V_C(0) = V_{C0}$
 $V_C(\infty) = V_{C0} \Rightarrow C_1 = V_{C0} - K_2$

Exercise can.gyrobodium

For the circuit diagram below, perform a complete circuit analysis to solve for $v_o(t)$ if $V_s(t) = 0$. Let $v_C(t)|_{t=0} = 5$ V and $dv_C/dt|_{t=0} = 0$ V/s be the initial conditions. Assume the characteristic equation has distinct roots. Recommendation: due to the initial conditions being given in it, solve the differential equation in v_C .

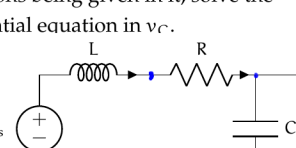


KCL $V_C = V_s$
 $i_L = i_R$ $i_R = i_C$ $i_L = i_C$
 KVL $V_s = V_L + V_R + V_C \Rightarrow V_C = V_s - V_R - V_L$
 Elemental Eq's
 $V_R = i_R R$

$\frac{dV_C}{dt} = \frac{1}{C} i_C \Rightarrow \frac{d^2 V_C}{dt^2} = \frac{1}{C} \frac{d i_C}{dt} = \frac{1}{C} \frac{d i_L}{dt}$
 $\frac{d^2 V_C}{dt^2} = \frac{1}{L} V_C = \frac{1}{L} (V_s - V_R - V_C) = \frac{1}{L} (V_s - i_C R - V_C)$
 $= \frac{1}{L} (V_s - i_C R - V_C)$

Exercise can.thyopptic

For the circuit diagram below, perform a complete circuit analysis to solve for $v_o(t)$ if $V_s(t) = 3 \sin(10t)$. Let $v_C(t)|_{t=0} = 0$ V and $dv_C/dt|_{t=0} = 0$ V/s be the initial conditions. Assume the characteristic equation has distinct, complex roots. Recommendation: due to the initial conditions being given in it, solve the differential equation in v_C . Also, consider which, if any, of your results from Exercise can. apply and reuse them, if so.

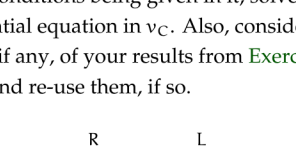


$\frac{d^3 V_C}{dt^3} = \frac{1}{LC} (V_s - i_C R - V_C)$
 $= \frac{1}{LC} (V_s - i_C R - V_C)$
 $= \frac{1}{LC} (V_s - RC \frac{dV_C}{dt} - V_C)$

$\frac{d^3 V_C}{dt^3} + \frac{R}{L} \frac{dV_C}{dt} + \frac{1}{LC} V_C = \frac{1}{LC} V_s = 0$
 $\lambda^3 + \frac{R}{L} \lambda + \frac{1}{LC} = 0$
 assume $\lambda = \lambda_1, \lambda_2, \lambda_3$ $\lambda_1 \neq \lambda_2$
 $V_C = C_1 e^{\lambda_1 t} + C_2 e^{\lambda_2 t} + C_3 e^{\lambda_3 t}$
 $V_C(0) = 5$ $\frac{dV_C}{dt}|_{t=0} = 0$
 $V_C(\infty) = C_1 + C_2 + C_3 = 5$
 $\frac{dV_C}{dt} = C_1 \lambda_1 e^{\lambda_1 t} + C_2 \lambda_2 e^{\lambda_2 t} + C_3 \lambda_3 e^{\lambda_3 t}$
 $\frac{dV_C}{dt}|_{t=0} = C_1 \lambda_1 + C_2 \lambda_2 + C_3 \lambda_3 = 0$

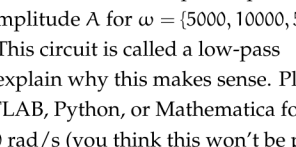Exercise can.hamogenesis

For the circuit diagram below, solve for $v_o(t)$ if $V_s(t) = A \sin \omega t$, where $A = 2$ V is the given amplitude and $\omega \in \mathbb{R}$ is a given angular frequency. Let $R = 50 \Omega$, $L = 50$ mH, and $C = 200$ nF. Let the circuit have initial conditions $v_C(0) = 1$ V and $i_L(0) = 0$ A. Find the steady-state ratio of the output amplitude to the input amplitude A for $\omega = \{5000, 10000, 50000\}$ rad/s. This circuit is called a low-pass filter—explain why this makes sense. Plot $v_o(t)$ in MATLAB, Python, or Mathematica for $\omega = 400$ rad/s (you think this won't be part of the quiz, but it will be!). Hint: either re-write your system of differential-algebraic equations and initial conditions as a single second-order differential equation with initial conditions in the differential variable or re-write it as a system of two first-order differential equations and solve that.




low-pass filter

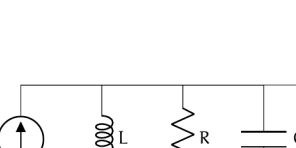Exercise can.photomicroscope

Use the circuit diagram below to answer the following questions and imperatives. Let $I_s = A_0$, where $A_0 > 0$ is a known constant. Perform a full circuit analysis, including the transient response. The initial inductor current is $i_L(0) = 0$ and the initial capacitor voltage is $v_C(0) = 0$. Assume the damping ratio $\zeta \in (0, 1)$; i.e. the system is underdamped and the roots of the characteristic equation are complex.

- Write the elemental, KCL, and KVL equations.
- Write the second-order differential equation for $i_L(t)$ arranged in the standard form and identify the natural frequency ω_n and damping ratio ζ .
- Convert the initial condition in v_C to a second initial condition in i_L .
- Solve the differential equation for $i_L(t)$ and use the solution to find the output voltage $v_o(t)$. It is acceptable to use a known solution and to express your solution in terms of ω_n and ζ .



—/20 p.

Steady-state circuit analysis does not require the, at times, lengthy process of solving differential equations. Impedance methods, presented in this chapter, are shortcuts to steady-state analysis. It is important to note that impedance methods do not give information about the transient response.