

nlmmul.exe Exercises for Chapter nlmmul

Exercice nlmmul01

Write a one- or two-sentence response to each of the following questions and imperatives. The use of equations is acceptable when they appear in a sentence. Don't quote me (use your own words, other than technical terminology).

- (a) Write the equivalent impedance of a resistor R and an inductor L in series. Express the result in rectangular and polar (phasor) form.
- (b) How do you find the Norton equivalent resistance?
- (c) Explain how a diode operates in forward-bias.
- (d) In a MOSFET, how much current will flow from the drain D to the source S when the gate-source voltage is 0.3 V ? Succinctly explain/justify.

Exercice nlmmul02

Write a one- or two-sentence response to each of the following questions and imperatives. The use of equations is acceptable when they appear in a sentence. Don't quote me (use your own words, other than technical terminology).

- (a) Describe a couple differences between MOSFETs and opamps.
- (b) If a DC source is connected to a circuit in steady state, describe an inductor in the circuit will be operating.
- (c) If a transformer increases an AC signal's voltage by a factor of 10; what happens to the signal's current?
- (d) How do we determine the diode resistance for the piecewise linear model of a diode?

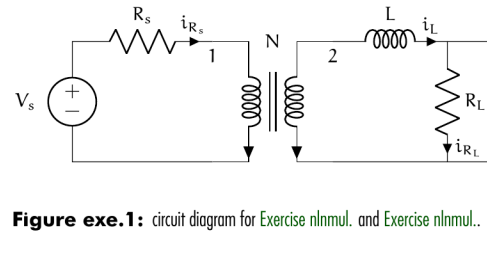


Figure exe.1: circuit diagram for Exercise nlmmul01 and Exercise nlmmul02.

Exercice nlmmul03

Write a one- or two-sentence response to each of the following questions and imperatives. The use of equations is acceptable when they appear in a sentence. Don't quote me (use your own words, other than technical terminology).

- (a) If the current through an inductor is suddenly switched off, what happens?
- (b) Let the output voltage of a resistor circuit be 5 V and the equivalent resistance 50Ω . What is the Thevenin equivalent circuit?
- (c) In the preceding part of this question, what is the Norton equivalent?
- (d) When can we use impedance analysis?

Exercice nlmmul04

For the circuit diagram of Fig. exe.1, solve for $v_o(t)$ if $V_s(t) = A \cos \omega t$. Let $N = n_2/n_1$, where n_1 and n_2 are the number of turns in each coil, 1 and 2, respectively. Also let $i_o(t) = i$ be the initial condition.

Exercice nlmmul05

Reads Exercise nlmmul01, but only consider the steady-state response. Use impedance methods!

Exercice nlmmul06

Calculate the current through a diode using the ideal model under the following conditions.

$$V_s = 5 \text{ A}, -3 \text{ V}$$

$$T = 38, 21, 28 \text{ }^\circ\text{C}$$

The diode can be assumed to have a saturation current of $I_s = 10^{-12} \text{ A}$. You may find the following helpful:

- Boltzmann constant: $1.38 \times 10^{-23} \frac{\text{J}}{\text{K}}$, and
- fundamental charge: $1.602 \times 10^{-19} \text{ C}$.

Exercice nlmmul07

When considering the steady state of circuits with only DC sources, all voltages and currents are constant and all diodes are in constant states (each is ON or OFF). The methods of Lec. nlmmul01a still apply, of course, but we needn't be concerned with a time evolution. Consider the circuits of Fig. exe.2. For each circuit, solve for the voltage across the $2 \text{ k}\Omega$ resistor. Treat each diode as an **ideal diode**.

Exercice nlmmul08

Repeat Exercise nlmmul01, but use the piecewise linear model of each diode.

Exercice nlmmul09

A diode clipping circuit is one that "clips" the tops and/or bottoms of a signal. These circuits can be used to set a maximum or minimum voltage for a signal. Consider the diode clipping circuit of Fig. exe.3. Source V_s effectively adjusts the maximum possible load voltage v_o , and V_2 the minimum. Let $V_s(t) = 5 \cos \omega t$, $V_1 = 5 \text{ V}$, $V_2 = -3 \text{ V}$, and $R_1 = R_2 = 50 \Omega$. Solve for $v_o(t)$. Use the ideal diode model.

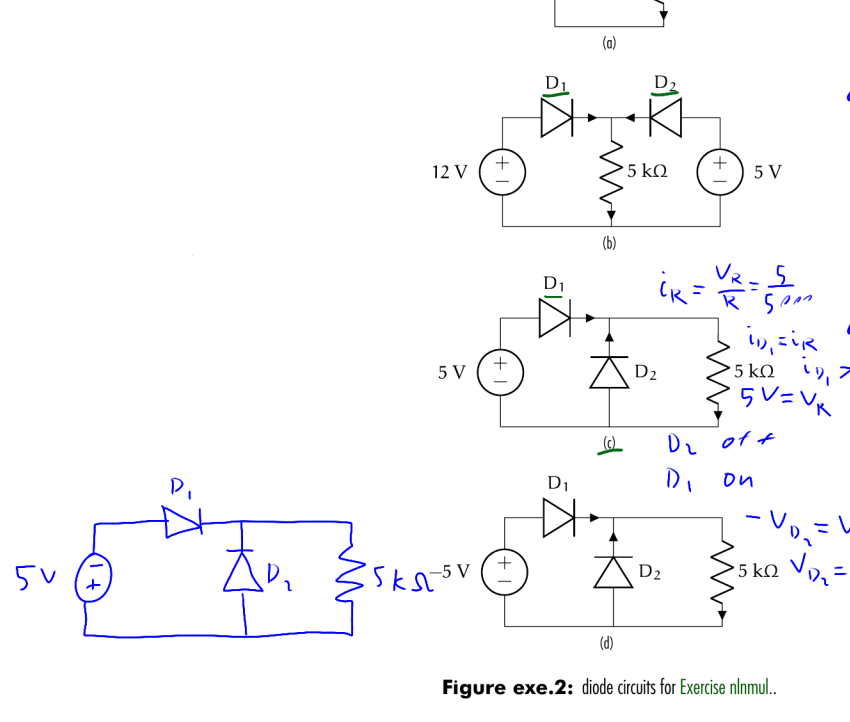


Figure exe.2: diode circuit for Exercise nlmmul09.

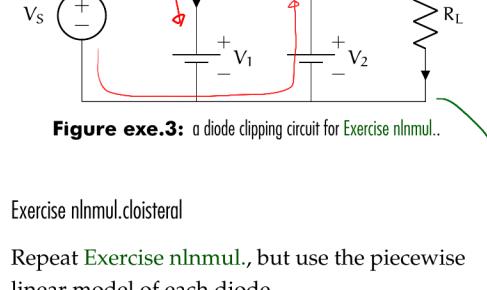


Figure exe.3: diode clipping circuit for Exercise nlmmul09.

Exercice nlmmul10

Repeat Exercise nlmmul01, but use the piecewise linear model of each diode.

Exercice nlmmul11

For the circuit diagram of Fig. exe.4, solve for $v_o(t)$ if $V_s(t) = A$ for some given $\Delta \geq 0.5 \text{ V}$. Let $v_o(t) = 0$ be the initial condition. Use the piecewise linear model for the diode with some $R_d \in R_{20}$. Do not estimate R_d .

Exercice nlmmul12

For the circuit shown in Fig. exe.5, determine the voltage across the load v_o in terms of parameters and the gate voltage source voltage V_g and V_2 . The parameters of the MOSFET are K and V_t . Assume MOSFET saturation operation.

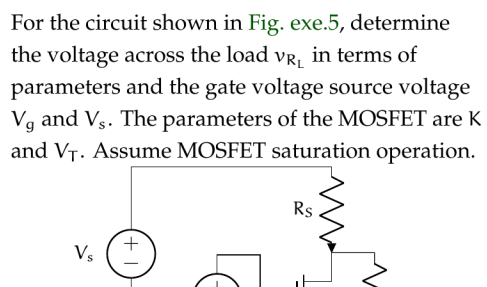


Figure exe.5: circuit for Exercise nlmmul12.

Exercice nlmmul13

The opamp circuit of Fig. exe.6 is used as a voltage-controlled current source for the load R_L . Show that it behaves as a current source with current i_o , controlled by voltage source v_i . Use two separate methods: (a) assuming $v_i = v_o$, and (b) not assuming $v_i = v_o$, rather, assuming the open loop gain of the opamp A is large. Comment on the differences between the methods of (a) and (b).

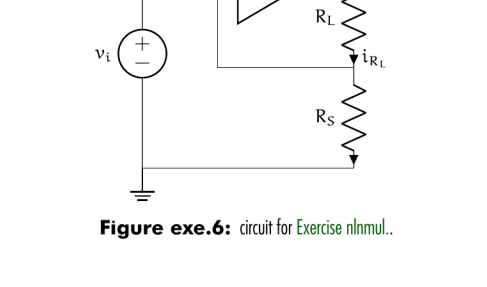


Figure exe.6: circuit for Exercise nlmmul13.

Exercice nlmmul14

Use the circuit diagram of Fig. exe.7 to answer the questions below. Use the sign convention from the diagram. Let $v_i = A \cos \omega t$ be an ac input voltage. The load Z_L impedance is not given.

- (a) Write the elemental equations in terms of Z_e , Z_c , Z_o , and Z_L (the impedances of the components).
- (b) Write the KCL and KVL equations.
- (c) Solve for the steady-state $v_o(t)$ without inserting the values of the impedances (that is, leave it in terms of Z_e , Z_c , Z_o , and Z_L).

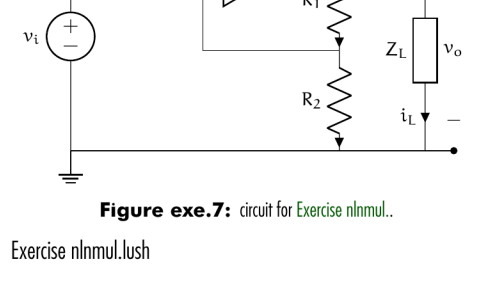


Figure exe.7: circuit for Exercise nlmmul14.

Exercice nlmmul15

Consider the circuit in Fig. exe.8. Solve for $v_o(t)$ for input voltage $v_i(t) = 5 \text{ V}$ sine wave of $v_i(t) = 5 \sin 25t$, and a sine wave of $v_i(t) = 5 \sin 252t$. Let $R_1 = 50 \Omega$, $R_2 = 10 \text{ k}\Omega$, $C = 10 \mu\text{F}$, and the opamp open-loop gain be $A = 10^5$. Let the initial condition be $v_c(t) = 0 \text{ V}$. In each case, plot the solution to show the transient response until it reaches steady-state.

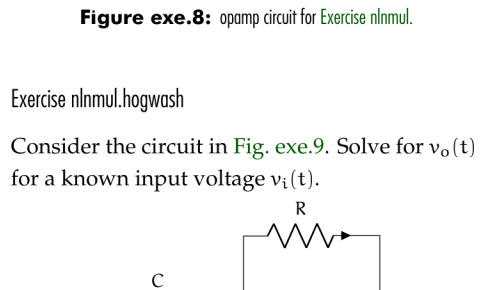


Figure exe.8: opamp circuit for Exercise nlmmul15.

Exercice nlmmul16

Consider the circuit in Fig. exe.9. Solve for $v_o(t)$ for a known input voltage $v_i(t)$.

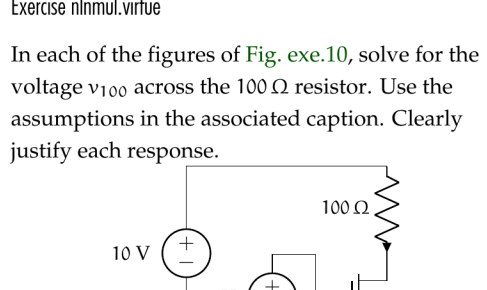


Figure exe.9: opamp circuit for Exercise nlmmul16.

Exercice nlmmul17

In each of the figures of Fig. exe.10, solve for the voltage v_{100} across the 100Ω resistor. Use the assumptions in the associated caption. Clearly justify each response.


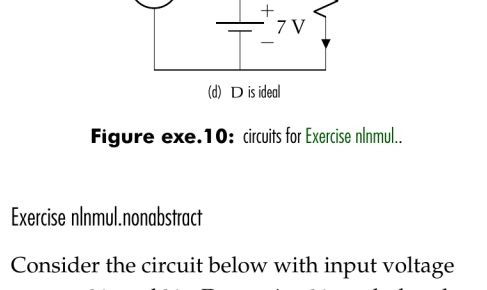


Figure exe.10: circuit for Exercise nlmmul17.

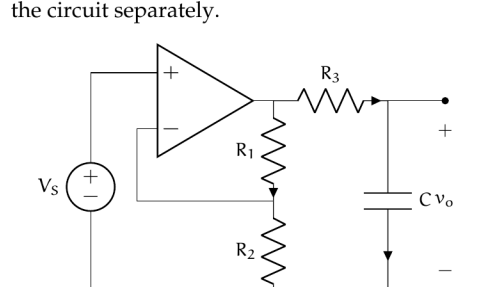
Exercice nlmmul18

Consider the circuit below with input voltage sources V_3 and V_4 . Determine V_5 such that the load voltage $v_o = 10 \text{ V}$. Let $R_1 = 2 \text{ k}\Omega$, $K = 0.5 \text{ mA/V}^2$, $V_t = 0.7 \text{ V}$, $V_3 = 20 \text{ V}$.



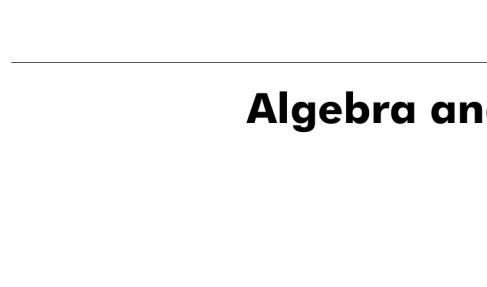Exercice nlmmul19

Consider the circuit below with input voltage source $V_3(t) = A$ where $A > 0$ is a known (but unspecified) constant. Perform a circuit analysis to solve for $v_o(t)$ for the initial condition $v_c(t) = 0$. Hint: It is easier if you realize the opamp output voltage is effectively an ideal voltage source (so it does not depend on v_o and v_c) and you can therefore treat the two parts of the circuit separately.



diode clipping circuit

3 V source, $5 \text{ k}\Omega$ resistor, diode D_1 .

3 V source, $5 \text{ k}\Omega$ resistor, diode D_1 , $5 \text{ k}\Omega$ resistor, diode D_2 .

$v_o = 0$
 $v_o > 0$
 $v_o < 0$

$v_o = \frac{5 \cos \omega t}{5000} = 0.001 \cos \omega t$
 $i_R = \frac{v_o}{R} = \frac{0.001 \cos \omega t}{5000} > 0$
 $i_R = i_o > 0 \checkmark$

KVL
 $3 = 0.1 + V_{Rd} + V_K$
KCL
 $i_o = i_{Rd} = i_K$
Elemental
 $V_{Rd} = i_{Rd} R_d$
 $V_K = i_K R_K$
 $V_K = i_K R_K$

$V_K = 3 - 0.1 - V_{Rd}$
 $= 3 - 0.1 - i_K R_d$
 $= 3 - 0.1 - i_K R_d$
 $= 3 - 0.1 - i_K \frac{R_d}{R_K}$
 $V_K + V_K \frac{R_d}{R_K} = 3 - 0.1$
 $V_K (1 + \frac{R_d}{R_K}) = 3 - 0.1$
 $V_K = (3 - 0.1) \frac{R_K}{R_K + R_d}$
 $= (3 - 0.1) \frac{5000}{5000 + 5000}$

diode clipping circuit

12 V source, $5 \text{ k}\Omega$ resistor, diode D_1 , $5 \text{ k}\Omega$ resistor, diode D_2 .

$v_o = 12 \text{ V}$
 $v_o = -7 \text{ V} < 0 \checkmark$
 $V_K = 12 \text{ V}$
 $i_{D1} = i_{Rd} = \frac{V_K}{R_K} = \frac{12}{5 \text{ k}} > 0 \checkmark$

$V_{Rd} = \frac{R_d}{R_d + R_L} V_i$
 $V_o = \frac{R_L}{R_d + R_L} V_i$
 otherwise

diode clipping circuit

12 V source, $5 \text{ k}\Omega$ resistor, diode D_1 , $5 \text{ k}\Omega$ resistor, diode D_2 , $5 \text{ k}\Omega$ resistor, diode D_3 .

$v_o = 12 \text{ V}$
 $v_o = -7 \text{ V} < 0 \checkmark$
 $V_K = 12 \text{ V}$
 $i_{D1} = i_{Rd} = \frac{V_K}{R_K} = \frac{12}{5 \text{ k}} > 0 \checkmark$

$V_{Rd} = \frac{R_d}{R_d + R_L} V_i$
 $V_o = \frac{R_L}{R_d + R_L} V_i$
 otherwise

diode clipping circuit

12 V source, $5 \text{ k}\Omega$ resistor, diode D_1 , $5 \text{ k}\Omega$ resistor, diode D_2 , $5 \text{ k}\Omega$ resistor, diode D_3 .

$v_o = 12 \text{ V}$
 $v_o = -7 \text{ V} < 0 \checkmark$
 $V_K = 12 \text{ V}$
 $i_{D1} = i_{Rd} = \frac{V_K}{R_K} = \frac{12}{5 \text{ k}} > 0 \checkmark$

$V_{Rd} = \frac{R_d}{R_d + R_L} V_i$
 $V_o = \frac{R_L}{R_d + R_L} V_i$
 otherwise