

```
syms ZL ZR1 ZR2 real
```

```
Ze = 1 / (1 / ZL + 1 / ZR2)
```

```
Ze =
```

$$\frac{1}{\frac{1}{ZL} + \frac{1}{ZR_2}}$$

```
Z = Ze / (Ze + ZR1)
```

```
Z =
```

$$\frac{1}{\left(\frac{1}{ZL} + \frac{1}{ZR_2}\right) \left(ZR_1 + \frac{1}{\frac{1}{ZL} + \frac{1}{ZR_2}}\right)}$$

```
syms R1 R2 L w real
```

```
Z = subs(Z, ZR1, R1)
```

```
Z =
```

$$\frac{1}{\left(\frac{1}{ZL} + \frac{1}{ZR_2}\right) \left(R_1 + \frac{1}{\frac{1}{ZL} + \frac{1}{ZR_2}}\right)}$$

```
Z = subs(Z, ZR2, R2)
```

```
Z =
```

$$\frac{1}{\left(\frac{1}{R_2} + \frac{1}{ZL}\right) \left(R_1 + \frac{1}{\frac{1}{R_2} + \frac{1}{ZL}}\right)}$$

```
Z = subs(Z, ZL, i * w * L)
```

```
Z =
```

$$\frac{1}{\left(R_1 + \frac{1}{\frac{1}{R_2} - \frac{i}{Lw}}\right) \left(\frac{1}{R_2} - \frac{i}{Lw}\right)}$$

```
a = simplify(real(Z))
```

```
a =
```

$$\frac{L^2 R_2 w^2 (R_1 + R_2)}{L^2 R_1^2 w^2 + 2 L^2 R_1 R_2 w^2 + L^2 R_2^2 w^2 + R_1^2 R_2^2}$$

b = simplify(imag(Z))

b =

$$\frac{L R_1 R_2^2 w}{L^2 R_1^2 w^2 + 2 L^2 R_1 R_2 w^2 + L^2 R_2^2 w^2 + R_1^2 R_2^2}$$

a/b

ans =

$$\frac{L w (R_1 + R_2)}{R_1 R_2}$$