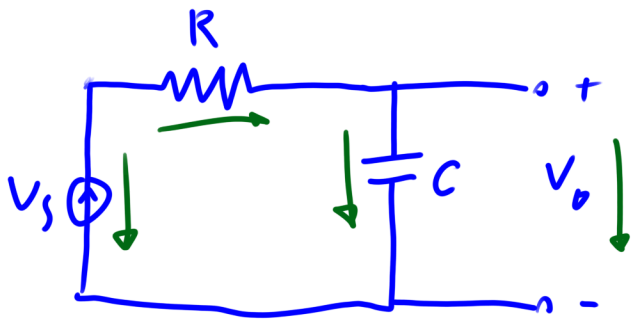


State Space Representation to ODE

RC circuit



$$0 = V_c - V_o \implies V_c = V_o$$

solve via

1. Differential eq'n

2. Normal tree to SS

State space to ODE

1. Differential eq'n

Elemental $\frac{dV_c}{dt} = \frac{1}{C} i_c$

$$V_R = R i_R \implies i_R = \frac{V_R}{R}$$


KVL $V_s = V_R + V_c \implies V_c = V_o$

KCL $i_R = i_c \implies V_R = V_s - V_c$

$$\frac{dV_c}{dt} = \frac{1}{C} i_c = \frac{1}{C} i_R = \frac{1}{RC} V_R = \frac{V_s - V_c}{RC}$$

$$\frac{dV_c}{dt} + \frac{1}{RC} V_c = \frac{1}{RC} V_s$$

2. Linear graph to SS

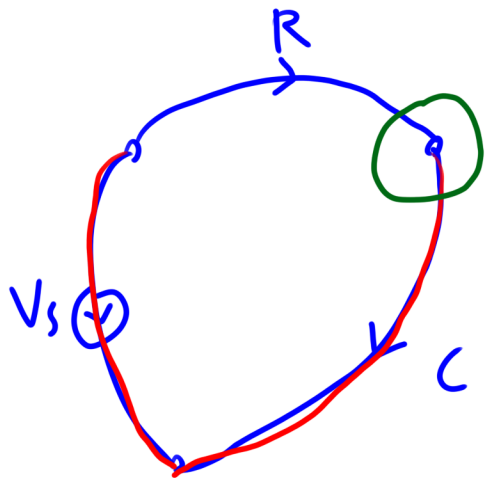

Primary: V_s V_c i_R

Secondary: I_s i_c V_R

State: V_c $n=1$

$$x = [V_c] \quad y = [V_c] \quad u = [V_s]$$

Elemental

$$\frac{dV_c}{dt} = \frac{1}{C} i_c = \frac{1}{C} i_R = \frac{V_s - V_c}{RC}$$

$$i_R = \frac{1}{R} V_R = \frac{V_s - V_c}{R}$$

Continuity

$$i_c = i_R$$

Compatibility

$$V_R = V_s - V_c$$

$$\dot{x} = \underbrace{\begin{bmatrix} -1 \\ RC \end{bmatrix}}_A x + \underbrace{\begin{bmatrix} 1 \\ RC \end{bmatrix}}_B u$$

$$y = \underbrace{[1]}_C x + \underbrace{[0]}_D u$$

SS to TF

$$\begin{aligned} H(s) &= C (sI - A)^{-1} B + D = 1 \left(s - \frac{-1}{RC} \right)^{-1} \frac{1}{RC} + 0 \\ &= \left(s + \frac{1}{RC} \right)^{-1} \frac{1}{RC} \\ &= \frac{1}{s + \frac{1}{RC}} \frac{1}{RC} \\ &= \frac{1}{RCs + 1} = \frac{Y(s)}{U(s)} \end{aligned}$$

$$\frac{RC \frac{dV_c}{dt} + V_c}{RC} = \frac{V_s}{RC}$$

$$\frac{dV_c}{dt} + \frac{1}{RC} V_c = \frac{1}{RC} V_s \quad \checkmark$$