

**nlmmul.exe Exercises for Chapter nlmmul**

**Exercice nlmmul00000**

Write a one- or two-sentence response to each of the following questions and imperatives. The use of equations is acceptable when they appear in a sentence. Don't quote me (use your own words, other than technical terminology).

- (a) Write the equivalent impedance of a resistor  $R$  and an inductor  $L$  in series. Express the result in rectangular and polar (phasor) form.
- (b) How do you find the Norton equivalent resistance?
- (c) Explain how a diode operates in forward-bias.
- (d) In a MOSFET, how much current will flow from the drain  $D$  to the source  $S$  when the gate-source voltage is  $0.3 \text{ V}$ ? Succinctly explain/justify.

**Exercice nlmmul00001**

Write a one- or two-sentence response to each of the following questions and imperatives. The use of equations is acceptable when they appear in a sentence. Don't quote me (use your own words, other than technical terminology).

- (a) Describe a couple differences between MOSFETs and opamps.
- (b) If a DC source is connected to a circuit in steady state, describe how an inductor in the circuit will be operating.
- (c) If a transformer increases an AC signal's voltage by a factor of  $10$ , what happens to the signal's current?
- (d) How do we determine the diode resistance for the piecewise linear model of a diode?

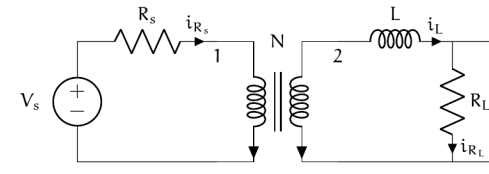


Figure exe.1: circuit diagram for Exercise nlmmul00001 and Exercise nlmmul00002.

**Exercice nlmmul00002**

Write a one- or two-sentence response to each of the following questions and imperatives. The use of equations is acceptable when they appear in a sentence. Don't quote me (use your own words, other than technical terminology).

- (a) If the current through an inductor is suddenly switched off, what happens?
- (b) Let the output voltage of a resistor circuit be  $5 \text{ V}$  and the equivalent resistance  $50 \Omega$ . What is the Thevenin equivalent circuit?
- (c) In the preceding part of this question, what is the Norton equivalent?
- (d) When can we use impedance analysis?

**Exercice nlmmul00003**

For the circuit diagram of Fig. exe.1, solve for  $v_o(t)$  if  $V_s(t) = A \cos \omega t$ . Let  $N = n_2/n_1$ , where  $n_1$  and  $n_2$  are the number of turns in each coil,  $1$  and  $2$ , respectively. Also let  $i_o(0^-) = 0$  be the initial condition.

**Exercice nlmmul00004**

Reads Exercise nlmmul00003, but only consider the steady-state response. Use impedance methods!

**Exercice nlmmul00005**

Calculate the current through a diode using the ideal model under the following conditions.

- $v_D = 5.8 \text{ V}$
- $T = 38.21, 28^\circ \text{C}$ .

The diode can be assumed to have a saturation current of  $I_s = 10^{-12} \text{ A}$ . You may find the following helpful.

- Boltzmann constant:  $1.381 \times 10^{-23} \frac{\text{J}}{\text{K}}$ , and
- fundamental charge:  $1.602 \times 10^{-19} \text{ C}$ .

**Exercice nlmmul00006**

When considering the steady state of circuits with only DC sources, all voltages and currents are constant and all diodes are in constant states (each is ON or OFF). The methods of Lec. nlmmul00001 still apply, of course, but we needn't be concerned with a time evolution. Consider the circuits of Fig. exe.2. For each circuit, solve for the voltage across the  $5 \text{ k}\Omega$  resistor. Treat each diode as an ideal diode.

**Exercice nlmmul00007**

Repeat Exercise nlmmul00006, but use the piecewise linear model of each diode.

**Exercice nlmmul00008**

A diode clipping circuit is one that "clips" the tops and/or bottoms of a signal. These circuits can be used to set a maximum or minimum voltage for a signal. Consider the diode clipping circuit of Fig. exe.3. Source  $V_1$  effectively adjusts the maximum possible load voltage  $v_{L2}$  and  $V_2$  the minimum. Let  $V_{D1} = 12 \text{ V}$  and  $V_{D2} = 5 \text{ V}$ ,  $V_1 = -3 \text{ V}$ , and  $R_1 = R_2 = 50 \Omega$ . Solve for  $v_{L2}(t)$ . Use the ideal diode model.

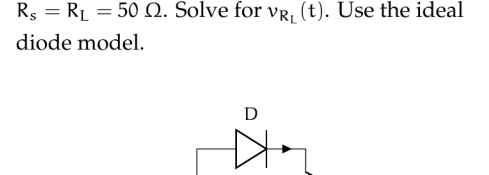


Figure exe.2: diode circuit for Exercise nlmmul00006.

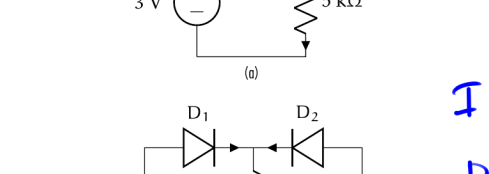


Figure exe.3: diode clipping circuit for Exercise nlmmul00008.

**Exercice nlmmul00009**

Repeat Exercise nlmmul00007, but use the piecewise linear model of each diode.

**Exercice nlmmul00010**

For the circuit diagram of Fig. exe.4, solve for  $v_o(t)$  if  $V_s(t) = A$  for some given  $A > 0.5 \text{ V}$ . Let  $v_o(0^-) = 0 \text{ V}$  be the initial condition. Use a piecewise linear model for the diode with some  $R_d \in \mathbb{R}_{>0}$ . Do not estimate  $R_d$ .

**Exercice nlmmul00011**

For the circuit shown in Fig. exe.5, determine the voltage across the load  $v_{L2}$  in terms of parameters and the gate voltage source voltage  $V_g$  and  $V_s$ . The parameters of the MOSFET are  $K$  and  $V_{gs}$ . Assume MOSFET saturation operation.

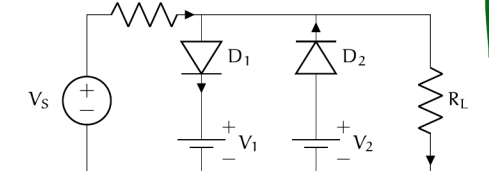


Figure exe.5: circuit for Exercise nlmmul00011.

**Exercice nlmmul00012**

The opamp circuit of Fig. exe.6 is used as a voltage-controlled current source for the load  $R_L$ . Show that it behaves as a current source with current  $i_{L2}$  controlled by voltage source  $v_1$ . Use two separate methods: (a) assuming  $v_1 = v_2$ , and (b) not assuming  $v_1 = v_2$ , rather, assuming the open loop gain of the opamp  $A$  is large. Comment on the differences between the methods of (a) and (b).

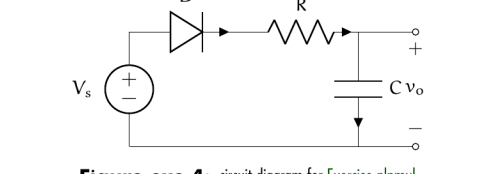


Figure exe.6: circuit for Exercise nlmmul00012.

**Exercice nlmmul00013**

Use the circuit diagram of Fig. exe.7 to answer the questions below. Use the sign convention from the diagram. Let  $v_1 = A \sin \omega t$  be an ac input voltage. The load  $Z_L$  impedance is not given.

- (a) Write the elemental equations in terms of  $Z_L$ ,  $Z_{R1}$ ,  $Z_{R2}$ , and  $Z_L$  (the impedances of the components).
- (b) Write the KCL and KVL equations.
- (c) Solve for the steady-state  $v_o(t)$  without inserting the values of the impedances (that is, leave it in terms of  $Z_L$ ,  $Z_{R1}$ ,  $Z_{R2}$ , and  $Z_L$ ).

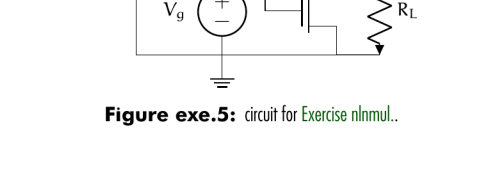


Figure exe.7: circuit for Exercise nlmmul00013.

**Exercice nlmmul00014**

Consider the circuit in Fig. exe.8. Solve for  $v_o(t)$  for input voltage  $v_1(t) = 5 \text{ V}$  sine wave of  $v_1(t) = 5 \sin 25t$ , and a sine wave of  $v_1(t) = 5 \sin 2525t$ . Let  $R_1 = 50 \Omega$ ,  $R_2 = 10 \text{ k}\Omega$ ,  $C = 10 \mu\text{F}$ , and the opamp open-loop gain be  $A = 10^5$ . Let the initial condition be  $v_c(0^-) = 0 \text{ V}$ . In each case, plot the solution to show the transient response until it reaches steady-state.

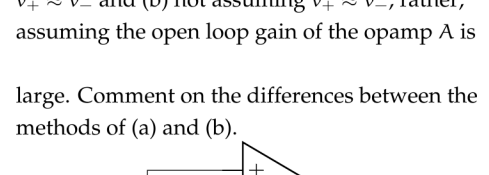


Figure exe.8: opamp circuit for Exercise nlmmul00014.

**Exercice nlmmul00015**

Consider the circuit in Fig. exe.9. Solve for  $v_o(t)$  for a known input voltage  $v_1(t)$ .

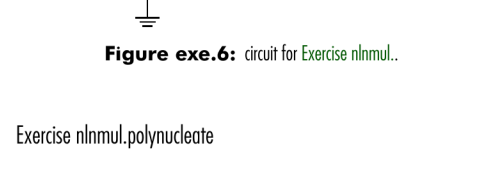


Figure exe.9: opamp circuit for Exercise nlmmul00015.

**Exercice nlmmul00016**

In each of the figures of Fig. exe.10, solve for the voltage  $v_{100}$  across the  $100 \Omega$  resistor. Use the assumptions in the associated caption. Clearly justify each response.

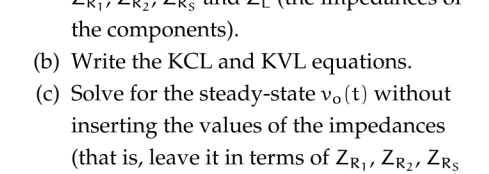


Figure exe.10: circuit for Exercise nlmmul00016.

**Exercice nlmmul00017**

Consider the circuit below with input voltage sources  $V_3$  and  $V_4$ . Determine  $V_5$  such that the load voltage  $v_{L2} = 10 \text{ V}$ . Let  $R_1 = 2 \text{ k}\Omega$ ,  $K = 0.5 \text{ mA/V}^2$ ,  $V_1 = 0.7 \text{ V}$ ,  $V_2 = 20 \text{ V}$ .

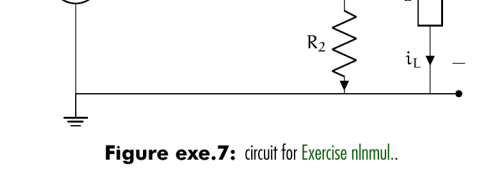


Figure exe.10: circuit for Exercise nlmmul00017.

**Exercice nlmmul00018**

Consider the circuit below with input voltage source  $V_1(t) = A$  where  $A > 0$  is a known (but unspecified) constant. Perform a circuit analysis to solve for  $v_o(t)$  for the initial condition  $v_c(0^-) = 0$ . Hint: It is easier if you realize the opamp output voltage is effectively an ideal voltage source (so it does not depend on  $v_1$  and  $v_2$ ) and you can therefore treat the two parts of the circuit separately.

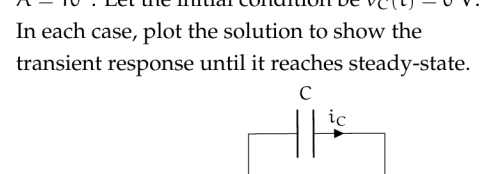


Figure exe.10: circuit for Exercise nlmmul00018.

**Exercice nlmmul00019**

Consider the circuit below with input voltage source  $V_1(t) = A$  where  $A > 0$  is a known (but unspecified) constant. Perform a circuit analysis to solve for  $v_o(t)$  for the initial condition  $v_c(0^-) = 0$ . Hint: It is easier if you realize the opamp output voltage is effectively an ideal voltage source (so it does not depend on  $v_1$  and  $v_2$ ) and you can therefore treat the two parts of the circuit separately.

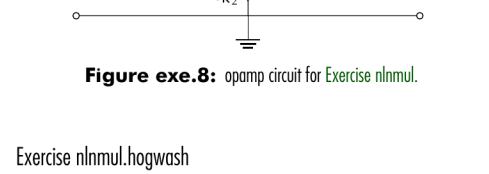


Figure exe.10: circuit for Exercise nlmmul00019.

**Exercice nlmmul00020**

Consider the circuit below with input voltage source  $V_1(t) = A$  where  $A > 0$  is a known (but unspecified) constant. Perform a circuit analysis to solve for  $v_o(t)$  for the initial condition  $v_c(0^-) = 0$ . Hint: It is easier if you realize the opamp output voltage is effectively an ideal voltage source (so it does not depend on  $v_1$  and  $v_2$ ) and you can therefore treat the two parts of the circuit separately.

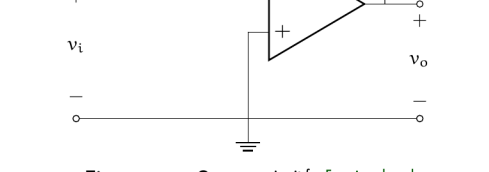


Figure exe.10: circuit for Exercise nlmmul00020.

**Exercice nlmmul00021**

Consider the circuit below with input voltage source  $V_1(t) = A$  where  $A > 0$  is a known (but unspecified) constant. Perform a circuit analysis to solve for  $v_o(t)$  for the initial condition  $v_c(0^-) = 0$ . Hint: It is easier if you realize the opamp output voltage is effectively an ideal voltage source (so it does not depend on  $v_1$  and  $v_2$ ) and you can therefore treat the two parts of the circuit separately.

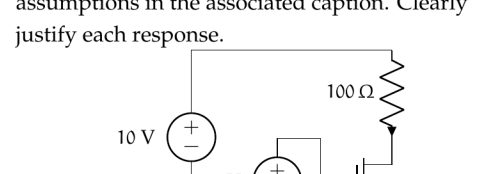


Figure exe.10: circuit for Exercise nlmmul00021.

**Exercice nlmmul00022**

Consider the circuit below with input voltage source  $V_1(t) = A$  where  $A > 0$  is a known (but unspecified) constant. Perform a circuit analysis to solve for  $v_o(t)$  for the initial condition  $v_c(0^-) = 0$ . Hint: It is easier if you realize the opamp output voltage is effectively an ideal voltage source (so it does not depend on  $v_1$  and  $v_2$ ) and you can therefore treat the two parts of the circuit separately.

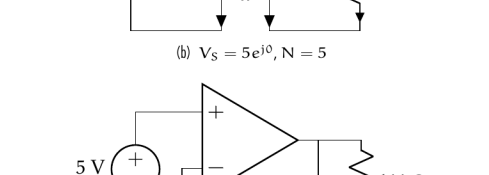


Figure exe.10: circuit for Exercise nlmmul00022.

**Exercice nlmmul00023**

Consider the circuit below with input voltage source  $V_1(t) = A$  where  $A > 0$  is a known (but unspecified) constant. Perform a circuit analysis to solve for  $v_o(t)$  for the initial condition  $v_c(0^-) = 0$ . Hint: It is easier if you realize the opamp output voltage is effectively an ideal voltage source (so it does not depend on  $v_1$  and  $v_2$ ) and you can therefore treat the two parts of the circuit separately.

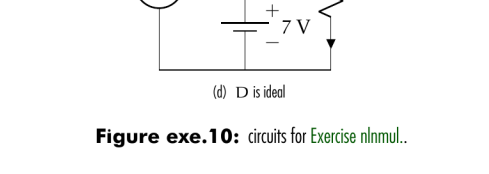


Figure exe.10: circuit for Exercise nlmmul00023.

**Exercice nlmmul00024**

Consider the circuit below with input voltage source  $V_1(t) = A$  where  $A > 0$  is a known (but unspecified) constant. Perform a circuit analysis to solve for  $v_o(t)$  for the initial condition  $v_c(0^-) = 0$ . Hint: It is easier if you realize the opamp output voltage is effectively an ideal voltage source (so it does not depend on  $v_1$  and  $v_2$ ) and you can therefore treat the two parts of the circuit separately.

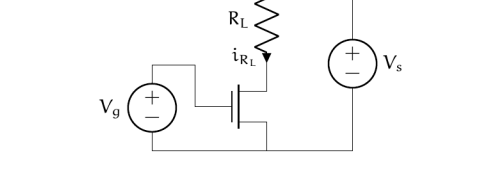


Figure exe.10: circuit for Exercise nlmmul00024.

**Exercice nlmmul00025**

Consider the circuit below with input voltage source  $V_1(t) = A$  where  $A > 0$  is a known (but unspecified) constant. Perform a circuit analysis to solve for  $v_o(t)$  for the initial condition  $v_c(0^-) = 0$ . Hint: It is easier if you realize the opamp output voltage is effectively an ideal voltage source (so it does not depend on  $v_1$  and  $v_2$ ) and you can therefore treat the two parts of the circuit separately.

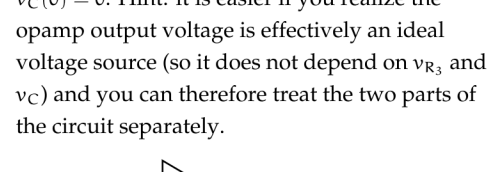


Figure exe.10: circuit for Exercise nlmmul00025.

**Exercice nlmmul00026**

Consider the circuit below with input voltage source  $V_1(t) = A$  where  $A > 0$  is a known (but unspecified) constant. Perform a circuit analysis to solve for  $v_o(t)$  for the initial condition  $v_c(0^-) = 0$ . Hint: It is easier if you realize the opamp output voltage is effectively an ideal voltage source (so it does not depend on  $v_1$  and  $v_2$ ) and you can therefore treat the two parts of the circuit separately.

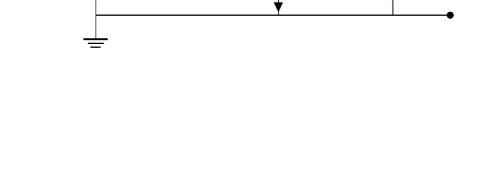


Figure exe.10: circuit for Exercise nlmmul00026.

**Exercice nlmmul00027**

Consider the circuit below with input voltage source  $V_1(t) = A$  where  $A > 0$  is a known (but unspecified) constant. Perform a circuit analysis to solve for  $v_o(t)$  for the initial condition  $v_c(0^-) = 0$ . Hint: It is easier if you realize the opamp output voltage is effectively an ideal voltage source (so it does not depend on  $v_1$  and  $v_2$ ) and you can therefore treat the two parts of the circuit separately.



Figure exe.10: circuit for Exercise nlmmul00027.

**Exercice nlmmul00028**

Consider the circuit below with input voltage source  $V_1(t) = A$  where  $A > 0$  is a known (but unspecified) constant. Perform a circuit analysis to solve for  $v_o(t)$  for the initial condition  $v_c(0^-) = 0$ . Hint: It is easier if you realize the opamp output voltage is effectively an ideal voltage source (so it does not depend on  $v_1$  and  $v_2$ ) and you can therefore treat the two parts of the circuit separately.



Figure exe.10: circuit for Exercise nlmmul00028.

**Exercice nlmmul00029**

Consider the circuit below with input voltage source  $V_1(t) = A$  where  $A > 0$  is a known (but unspecified) constant. Perform a circuit analysis to solve for  $v_o(t)$  for the initial condition  $v_c(0^-) = 0$ . Hint: It is easier if you realize the opamp output voltage is effectively an ideal voltage source (so it does not depend on  $v_1$  and  $v_2$ ) and you can therefore treat the two parts of the circuit separately.



Figure exe.10: circuit for Exercise nlmmul00029.

**Exercice nlmmul00030**

Consider the circuit below with input voltage source  $V_1(t) = A$  where  $A > 0$  is a known (but unspecified) constant. Perform a circuit analysis to solve for  $v_o(t)$  for the initial condition  $v_c(0^-) = 0$ . Hint: It is easier if you realize the opamp output voltage is effectively an ideal voltage source (so it does not depend on  $v_1$  and  $v_2$ ) and you can therefore treat the two parts of the circuit separately.



Figure exe.10: circuit for Exercise nlmmul00030.