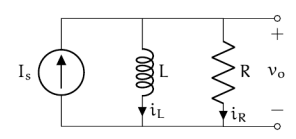


**can.exe Exercises for Chapter can**

Exercise can.mod

Use the diagram below to answer the following questions and imperatives. Let  $I_s = A_0$ , where  $A_0 \in \mathbb{R}$  is a known constant. Perform a full circuit analysis, including the transient response. The initial inductor current is  $i_L(0) = 0$ .


- Write the elemental, KCL, and KVL equations.
- Write the differential equation for  $i_L(t)$  arranged in the standard form and identify the time constant  $\tau$ .
- Solve the differential equation for  $i_L(t)$  and use the solution to find the output voltage  $v_o(t)$ .



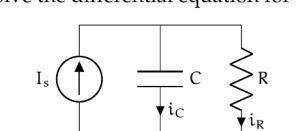Exercise can.theoretically


Use the diagram below to answer the following questions and imperatives. Let  $I_s = A_0$ , where  $A_0 \in \mathbb{R}$  is a known constant. Perform a full circuit analysis, including the transient response. The initial capacitor voltage is  $v_C(0) = v_{C0}$ , a known constant.

- Write the elemental, KCL, and KVL equations.
- Write the differential equation for  $v_C(t)$  arranged in the standard form.
- Solve the differential equation for  $v_C(t)$ .




Exercise can.hippophoto

For the RC circuit diagram below, perform a complete circuit analysis to solve for  $v_o(t)$  if  $V_s(t) = A \sin \omega t$ , where  $A \in \mathbb{R}$  is a given amplitude and  $\omega \in \mathbb{R}$  is a given angular frequency. Let  $v_C(t)|_{t=0} = v_{C0}$ , where  $v_{C0} \in \mathbb{R}$  is a given initial capacitor voltage. Hint: you will need to solve a differential equation for  $v_C(t)$ .

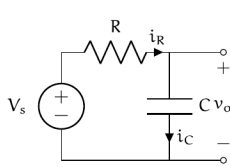


Exercise can.frustration

For the circuit diagram below, perform a complete circuit analysis to solve for  $v_o(t)$  if  $V_s(t) = A \sin \omega t$ , where  $A \in \mathbb{R}$  is a given amplitude and  $\omega \in \mathbb{R}$  is a given angular frequency. Let  $i_L(t)|_{t=0} = 0$  be the initial inductor current. Hint: you will need to solve a differential equation for  $i_L(t)$ .

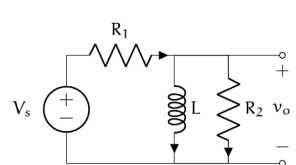


Exercise can.gyrobobium

For the circuit diagram below, perform a complete circuit analysis to solve for  $v_o(t)$  if  $V_s(t) = 0$ . Let  $v_C(t)|_{t=0} = 5$  V and  $\frac{dv_C}{dt}|_{t=0} = 0$  V/s be the initial conditions. Assume the characteristic equation has distinct roots. Recommendation: due to the initial conditions being given in it, solve the differential equation in  $v_C$ .

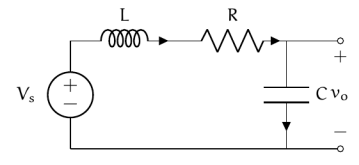

Exercise can.thyopptic

For the circuit diagram below, perform a complete circuit analysis to solve for  $v_o(t)$  if  $V_s(t) = 3 \sin(10t)$ . Let  $v_C(t)|_{t=0} = 0$  V and  $\frac{dv_C}{dt}|_{t=0} = 0$  V/s be the initial conditions. Assume the characteristic equation has distinct complex roots. Recommendation: due to the initial conditions being given in it, solve the differential equation in  $v_C$ . Also, consider which, if any, of your results from Exercise can. apply and re-use them, if so.

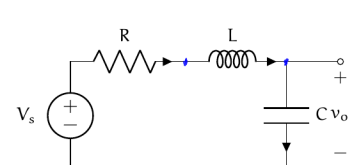

$$\frac{dv_C}{dt} = \frac{1}{C} I_s$$

$$V_o = V_C$$

$$V_o = V_R + V_L + V_C$$

$$\frac{d^2 v_C}{dt^2} + a_1 \frac{dv_C}{dt} + a_2 v_C = b_2 \sin(10t)$$


$$V_C = k_1 \sin(10t) + k_2 \cos(10t)$$

$$\frac{dv_C}{dt} = 10k_1 \cos(10t) - 10k_2 \sin(10t)$$

$$\frac{d^2 v_C}{dt^2} = -10^2 k_1 \sin(10t) - 10^2 k_2 \cos(10t)$$

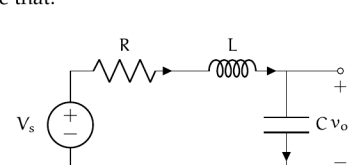Exercise can.hamogenesis

For the circuit diagram below, solve for  $v_o(t)$  if  $V_s(t) = A \sin \omega t$ , where  $A = 2$  V is the given amplitude and  $\omega \in \mathbb{R}$  is a given angular frequency. Let  $R = 50 \Omega$ ,  $L = 50$  mH, and  $C = 200$  nF. Let the circuit have initial conditions  $v_C(0) = 1$  V and  $i_L(0) = 0$  A. Find the steady-state ratio of the output amplitude to the input amplitude  $A$  for  $\omega = \{5000, 10000, 50000\}$  rad/s. This circuit is called a low-pass filter—explain why this makes sense. Plot  $v_o(t)$  in MATLAB, Python, or Mathematica for  $\omega = 400$  rad/s (you think this won't be part of the quiz, but it will be!). Hint: either re-write your system of differential-algebraic equations and initial conditions as a single second-order differential equation with initial conditions and solve that.



low-pass filter

$$\frac{dv_C}{dt} = \frac{1}{C} \frac{dI_s}{dt}$$

$$= \frac{1}{CL} (V_s - V_R - V_C) = \frac{1}{CL} (V_s - R I_s - V_C)$$

$$= \frac{1}{CL} (V_s - R C \frac{dv_C}{dt} - V_C)$$

$$\frac{d^2 v_C}{dt^2} + \frac{R}{L} \frac{dv_C}{dt} + \frac{1}{LC} v_C = \frac{1}{CL} 3 \sin(10t)$$

$$\lambda^2 + \frac{R}{L} \lambda + \frac{1}{LC} = 0 \Rightarrow \lambda = \lambda_1, \lambda_2 \quad \lambda_1 \neq \lambda_2$$

$$V_C = c_1 e^{\lambda_1 t} + c_2 e^{\lambda_2 t}$$

$$V_C = k_1 \sin(10t) + k_2 \cos(10t)$$


$$\frac{dv_C}{dt} = 10k_1 \cos(10t) - 10k_2 \sin(10t)$$

$$\frac{d^2 v_C}{dt^2} = -10^2 k_1 \sin(10t) - 10^2 k_2 \cos(10t)$$

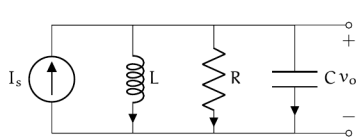Exercise can.photochromosome

Use the circuit diagram below to answer the following questions and imperatives. Let  $I_s = A_0$ , where  $A_0 > 0$  is a known constant. Perform a full circuit analysis, including the transient response. The initial inductor current is  $i_L(0) = 0$  and the initial capacitor voltage is  $v_C(0) = 0$ . Assume the damping ratio  $\zeta \in (0, 1)$ ; i.e. the system is underdamped and the roots of the characteristic equation are complex.

- Write the elemental, KCL, and KVL equations.
- Write the second-order differential equation for  $i_L(t)$  arranged in the standard form and identify the natural frequency  $\omega_n$  and damping ratio  $\zeta$ .
- Convert the initial condition in  $v_C$  to a second initial condition in  $i_L$ .
- Solve the differential equation for  $i_L(t)$  and use the solution to find the output voltage  $v_o(t)$ . It is acceptable to use a known solution and to express your solution in terms of  $\omega_n$  and  $\zeta$ .



—/20 p.

$$-10^2 k_1 - \frac{R}{L} 10 k_1 + \frac{1}{LC} k_1 = \frac{3}{CL}$$

$$-10^2 k_2 + \frac{R}{L} 10 k_2 + \frac{1}{LC} k_2 = 0$$

$$k_1 = \frac{\frac{3}{CL}}{\left(\frac{1}{LC} - 10^2\right)}$$

$$k_2 = \frac{\frac{3}{CL}}{\left(\frac{1}{LC} - 10^2\right) \left(\frac{R}{L}\right) - \frac{10^2}{CL}}$$

$$V_C = c_1 e^{\lambda_1 t} + c_2 e^{\lambda_2 t} + k_1 \sin(10t) + k_2 \cos(10t)$$

$$V_C(0) = 0 \quad \frac{dv_C}{dt} \Big|_{t=0} = 0$$

$$V_C(0) = c_1 + c_2 + k_1 = 0$$

$$\frac{dv_C}{dt} = c_1 \lambda_1 e^{\lambda_1 t} + c_2 \lambda_2 e^{\lambda_2 t} + 10k_1 \cos(10t) - 10k_2 \sin(10t)$$

$$\frac{dv_C}{dt} \Big|_{t=0} = c_1 \lambda_1 + c_2 \lambda_2 + 10k_1 = 0$$

Steady-state circuit analysis does not require the, at times, lengthy process of solving differential equations. Impedance methods, presented in this chapter, are shortcuts to steady-state analysis. It is important to note that impedance methods do not give information about the transient response.