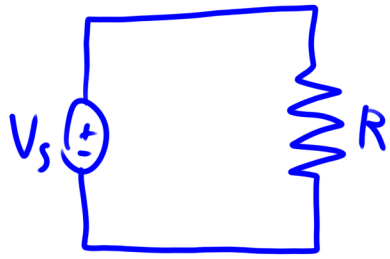


3.7. Consider an electric home heating system. A resistive element R is connected to the 110-volt, 60-Hz electric supply.

- (a) Determine the current flow through the element as a function of time.
 (b) Determine the average thermal power generated per cycle.
 (c) If the heater is rated at 1000 watts, what is the value of the heater resistance R ?

a)



$$V_s = \frac{110}{2} \sin(60(2\pi)t)$$

$$V_R = R i_R \quad V_R = V_s$$

$$i_R = \frac{V_R}{R} = \boxed{\frac{V_s}{R}}$$

b)
$$P(t) = V_R i_R = V_s \frac{V_s}{R} = \frac{V_s^2}{R}$$

$$P = \frac{1}{T} \int_0^T \frac{V_s^2}{R} dt = \frac{60}{R} \int_0^{1/60} V_s^2 dt$$

$$= \frac{60}{R} \frac{110^2}{4} \int_0^{1/60} \sin^2(120\pi t) dt$$

$$= \frac{181500}{R} \int_0^{1/60} \frac{1 - \cos(120\pi t)}{2} dt$$

$$= \frac{90750}{R} \left(t - \frac{\sin(120\pi t)}{120\pi} \right) \Big|_0^{1/60}$$

$$= \frac{90750}{R} t \Big|_0^{1/60} = \frac{90750}{60R} = \boxed{\frac{1512}{R} = P}$$

c)

$$1000 = \frac{1512}{R} \Rightarrow R = \frac{1512}{1000} = \boxed{1.51 \Omega}$$