


**Mechanical Engineering**  
**345 - Mechatronics**  
 Midterm Exam 1  
 Cameron Devine  
 14 October 2021

Directions: take-home, all day, open notes, open book. Calculators, MATLAB, etc. allowed. Use your own paper, work neatly, and clearly mark your answers. Partial credit may be given.

**Problem bugsul**

Write a one- or two-sentence response to each of the following questions and imperatives. The use of equations is acceptable when they appear in a sentence. Don't quote me (use your own words, other than technical terminology).

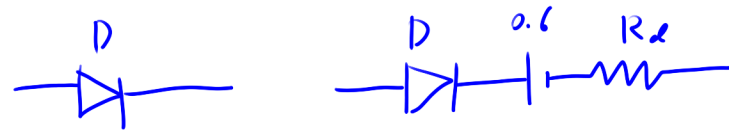- a. What is the piecewise linear diode model.
- b. What are the relationships between input and output voltage and current in a transformer? Why?
- c. The current through a capacitor becomes zero. What happens to the voltage across the capacitor?
- d. Explain the how the current from the drain to the source of a MOSFET changes as the gate voltage is varied. Assume the MOSFET is in the saturation region.
- e. When can we use impedance analysis?




$V_2 = N V_1$      $i_2 = \frac{-1}{N} i_1$      $P_1 = P_2$   
 $\frac{dV_c}{dt} = \frac{1}{C} i_c$     if  $i_c = 0$      $\frac{dV_c}{dt} = 0$      $V_c = \text{constant}$   
 $i_{D_S} = K (V_{GS} - V_T)^2$     if  $V_T$  is small  
 $i_{D_S} \propto V_{GS}^2$

**Problem reorientator**

Use the circuit diagram below to answer the following questions and imperatives. Let  $V_s = A \sin(\omega t)$ . Perform a full circuit analysis, including the transient response to find  $v_o(t)$ . The initial inductor current is  $i_L(0) = 0$  and the initial capacitor voltage  $v_c(0) = 0$ .

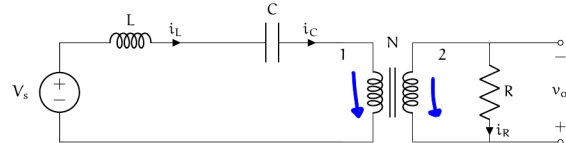
- a. Write the elemental, KCL, and KVL equations.
- b. Write the second-order differential equation for  $v_c(t)$  arranged in the standard form.
- c. Convert the initial condition in  $i_L$  to a second initial condition in  $v_c$ .
- d. Let  $R = 10 \text{ k}\Omega$ ,  $L = 100 \text{ mH}$ ,  $C = 100 \text{ }\mu\text{F}$ ,  $N = 5$ ,  $A = 5 \text{ V}$ , and  $\omega = 500 \text{ rad/s}$  and solve for  $v_c(t)$ .
- e. Derive an equation to find  $v_o(t)$  from  $v_c(t)$ . This equation will include derivatives of  $v_c(t)$ . You don't need to add your solution to part d into this equation.



**Problem unrectangularization**


Use the circuit diagram below to answer the following questions. Assume  $R_1 = R_2$  and that all diodes are ideal.

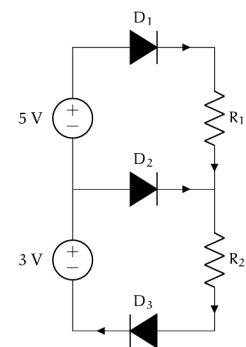- a. What state is each diode in?
- b. What is the voltage drop across each of the resistors?



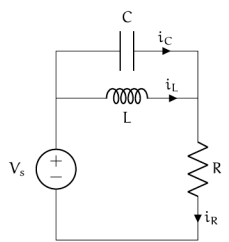
**Problem transmittationism**

For the circuit diagram below, perform a circuit analysis to solve for the steady state voltage across the resistor  $R$ ,  $v_R(t)$ . Assume  $V_s = A e^{j\omega t}$  in sine phasor form and  $A \in \mathbb{R}$ . Express your answer in sine phasor form.



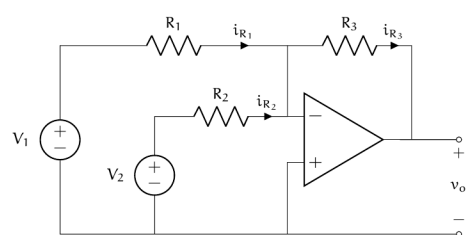**Problem kirfunkle**

Consider the circuit below with two constant voltage sources  $V_1$  and  $V_2$ . Find the steady state voltage output  $v_o$ , assuming  $R_1 = R_2 = R_3$ . Hint: start solving with the equation  $v_o = -v_{R_3}$ .



**KCL**  
 $i_{D1} = i_{R1}$   
 $i_{R1} + i_{D2} = i_{R2}$   
 $i_{R2} = i_{D3}$

**Elemental E2's**  
 $V_{R1} = i_{R1} R_1$   
 $V_{R2} = i_{R2} R_2$

**KVL**  
 $3 + 5 = V_{D1} + V_{R1} + V_{R2} + V_{D3}$   
 $3 = V_{D2} + V_{R2} + V_{D3}$

assume  $D_1$  on     $D_2$  off     $D_3$  on  
 $V_{D1} = 0$      $V_{D2} = 0$      $V_{D3} = 0$

$i_{D1} = i_{R1}$      $i_{R1} + i_{D2} = i_{R2}$   
 $i_{D1} = i_{R1} = i_{R2} = i_{D3}$

$3 = V_{D1} + V_{R1} + V_{R2} + V_{D3}$   
 $= i_{R1} R_1 + i_{R2} R_2 = i_{R2} (R_1 + R_2) = 2 i_{R2} R_2$

if  $R_2 \gg 0$  then  $i_{R2} \gg 0$

$i_{D1} \gg 0$      $i_{D3} \gg 0$

$3 = V_{D2} + V_{R2} + V_{D3}$

$V_{D2} = 3 - V_{R2} = 3 - 4 = -1 < 0$  ✓

$3 = 2 i_{R2} R_2 = 2 V_{R2}$

$4 = V_{R2}$

$3 = V_{R1} + V_{R2} = V_{R1} + 4$

$V_{R1} = 3 - 4 = -1$

a. Elemental E2's    KVL  
 $V_R = R i_R$      $V_S = V_L + V_C + V_1$   
 $\frac{dV_c}{dt} = \frac{1}{C} i_c$      $V_2 = V_R$   
 KCL  
 $\frac{d i_L}{dt} = \frac{1}{L} V_L$      $i_L = i_c = i_1$   
 $i_2 = -i_R$

b.  $\frac{dV_c}{dt} = \frac{1}{C} i_c = \frac{1}{C} i_L$

$\frac{d^2 V_c}{dt^2} = \frac{1}{C} \frac{d i_L}{dt} = \frac{1}{LC} V_L = \frac{1}{LC} (V_S - V_C - V_1)$   
 $= \frac{1}{LC} (V_S - V_C - \frac{1}{N} V_2) = \frac{1}{LC} (V_S - V_C - \frac{1}{N} V_R)$   
 $= \frac{1}{LC} (V_S - V_C - \frac{1}{N} R i_R)$   
 $= \frac{1}{LC} (V_S - V_C + \frac{R}{N} i_2) = \frac{1}{LC} (V_S - V_C - \frac{R}{N^2} i_1)$   
 $= \frac{1}{LC} (V_S - V_C - \frac{R}{N^2} i_c) = \frac{1}{LC} (V_S - V_C - \frac{R}{N^2} \frac{dV_c}{dt})$

$\frac{d^2 V_c}{dt^2} + \frac{R}{LN^2} \frac{dV_c}{dt} + \frac{1}{LC} V_c = \frac{1}{LC} V_S$

c.  $i_L = i_c = C \frac{dV_c}{dt}$   
 $i_L(0) = 0$      $\frac{dV_c}{dt} \Big|_{t=0} = 0$

e.  $V_o = V_R = V_2 = N V_1 = N (V_S - V_L - V_C)$   
 $= N (V_S - L \frac{d i_L}{dt} - V_C) = N (V_S - L \frac{d i_c}{dt} - V_C)$

$= N (V_S - LC \frac{d^2 V_c}{dt^2} - V_C)$