

Mechanical Engineering
345 - Mechatronics
 Midterm Exam 1
 Cameron Devine
 14 October 2021

Directions: take-home, all day, open notes, open book. Calculators, MATLAB, etc. allowed. Use your own paper, work neatly, and clearly mark your answers. Partial credit may be given.

Problem 1


Write a one- or two-sentence response to each of the following questions and imperatives. The use of equations is acceptable when they appear in a sentence. Don't quote me (use your own words, other than technical terminology). /10 p.

- a What is the piecewise linear diode model.
- b What are the relationships between input and output voltage and current in a transformer? Why?
- c The current through a capacitor becomes zero. What happens to the voltage across the capacitor?
- d Explain the how the current from the drain to the source of a MOSFET changes as the gate voltage is varied. Assume the MOSFET is in the saturation region.
- e When can we use impedance analysis?

Problem 2

Use the circuit diagram below to answer the following questions and imperatives. Let $V_s = A \sin(\omega t)$. Perform a full circuit analysis, including the transient response to find $v_C(t)$. The initial inductor current is $i_L(0) = 0$ and the initial capacitor voltage $v_C(0) = 0$. /40 p.


- a Write the elemental, KCL, and KVL equations.
- b Write the second-order differential equation for $v_C(t)$ arranged in the standard form.
- c Convert the initial condition in i_L to a second initial condition in v_C .
- d Let $R = 10 \text{ k}\Omega$, $L = 100 \text{ mH}$, $C = 100 \text{ }\mu\text{F}$, $N = 5$, $A = 5 \text{ V}$, and $\omega = 500 \text{ rad/s}$ and solve for $v_C(t)$.
- e Derive an equation to find $v_C(t)$ from $v_C(0)$. This equation will include derivatives of $v_C(t)$. You don't need to add your solution to part d into this equation.

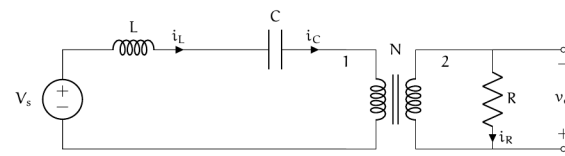

Problem 3



Use the circuit diagram below to answer the following questions. Assume $R_1 = R_2$ and that all diodes are ideal. /15 p.

- a What state is each diode in?
- b What is the voltage drop across each of the resistors?

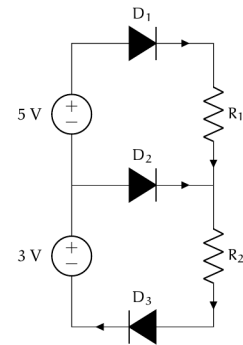

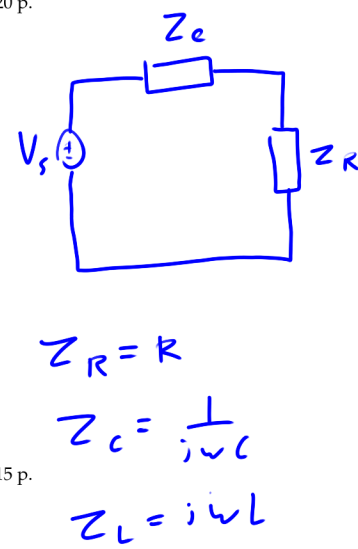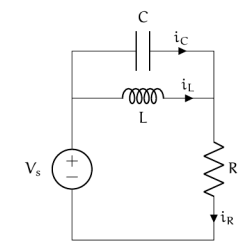Problem 4

For the circuit diagram below, perform a circuit analysis to solve for the steady state voltage across the resistor R , $v_R(t)$. Assume $V_s = A e^{j\omega t}$ in sine phasor form and $A \in \mathbb{R}$. Express your answer in sine phasor form. /20 p.



$$V_R = V_s \frac{Z_R}{Z_c + Z_R}$$

$$Z_c = \frac{1}{\frac{1}{Z_c} + \frac{1}{Z_L}} = \frac{1}{j\omega C + \frac{1}{j\omega L}} = \frac{j\omega L}{1 - \omega^2 LC}$$

$$V_R = V_s \frac{R}{\frac{j\omega L}{1 - \omega^2 LC} + R} = V_s \frac{R(1 - \omega^2 LC)}{j\omega L + R - \omega^2 RLC}$$

$$= V_s \frac{R^2 - \omega^2 R^2 LC - j\omega RL - \omega^2 R^2 LC + \omega^4 L^2 R^2 C^2 + j\omega^3 L^2 RC}{R^2 - 2\omega^2 R^2 LC + \omega^4 L^2 R^2 C^2 + \omega^2 L^2}$$

$$= V_s Z$$

$$\text{Re}(Z) = \frac{R^2 - 2\omega^2 R^2 LC + \omega^4 L^2 R^2 C^2}{R^2 - 2\omega^2 R^2 LC + \omega^4 L^2 R^2 C^2 + \omega^2 L^2}$$

$$\text{Im}(Z) = \frac{\omega^3 L^2 RC - \omega RL}{R^2 - 2\omega^2 R^2 LC + \omega^4 L^2 R^2 C^2 + \omega^2 L^2}$$

$$B = |Z| = \sqrt{\text{Re}(Z)^2 + \text{Im}(Z)^2}$$

$$= \frac{\sqrt{(R^2 - 2\omega^2 R^2 LC + \omega^4 L^2 R^2 C^2)^2 + (\omega^3 L^2 RC - \omega RL)^2}}{R^2 - 2\omega^2 R^2 LC + \omega^4 L^2 R^2 C^2 + \omega^2 L^2}$$

$$\phi = \tan^{-1} \left(\frac{\text{Im}(Z)}{\text{Re}(Z)} \right)$$

$$= \tan^{-1} \left(\frac{\omega^3 L^2 RC - \omega RL}{R^2 - 2\omega^2 R^2 LC + \omega^4 L^2 R^2 C^2} \right)$$

$$V_R = V_s Z = A e^{j\frac{\pi}{2}} B e^{j\phi} = A B e^{j(\frac{\pi}{2} + \phi)}$$

for lab

$$V_o = V_s Z(\omega)$$

$$\frac{V_o}{V_s} = |Z(\omega)|$$

KCL
 $i_{R1} + i_{R2} = i_{R3}$
 KVL
 $V_1 = V_{R1}$
 $V_2 = V_{R2}$
 $V_1 = V_{R1} + V_{R3} + V_o$
 $V_2 = V_{R2} + V_{R3} + V_o$
 $0 = V_{R3} + V_o$

Elemental Eq's
 $V_{R1} = R_1 i_{R1}$
 $V_{R2} = R_2 i_{R2}$
 $V_{R3} = R_3 i_{R3}$
 $V_+ = V_-$
 $i_+ = i_- = 0$
 $V_o = -V_{R3} = -R_3 i_{R3}$
 $= -R_3 (i_{R1} + i_{R2})$
 $= -R_3 \left(\frac{V_{R1}}{R_1} + \frac{V_{R2}}{R_2} \right)$
 $= -R_3 \left(\frac{V_1}{R_1} + \frac{V_2}{R_2} \right)$
 $= -(V_1 + V_2)$