

Mechanical Engineering
345 - Mechatronics
 Midterm Exam 1
 Cameron Devine
 14 October 2021

Directions: take-home, all day, open notes, open book. Calculators, MATLAB, etc. allowed. Use your own paper, work neatly, and clearly mark your answers. Partial credit may be given.

Problem bugsul


Write a one- or two-sentence response to each of the following questions and imperatives. The use of equations is acceptable when they appear in a sentence. Don't quote me (use your own words, other than technical terminology).

- a What is the piecewise linear diode model.
- b What are the relationships between input and output voltage and current in a transformer? Why?
- c The current through a capacitor becomes zero. What happens to the voltage across the capacitor?
- d Explain the how the current from the drain to the source of a MOSFET changes as the gate voltage is varied. Assume the MOSFET is in the saturation region.
- e When can we use impedance analysis?

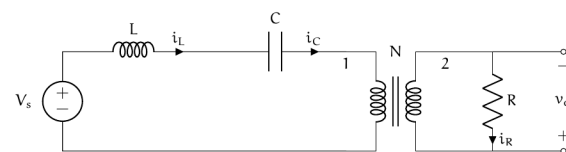Problem reorientator

Use the circuit diagram below to answer the following questions and imperatives. Let $V_s = A \sin(\omega t)$. Perform a full circuit analysis, including the transient response to find $v_o(t)$. The initial inductor current is $i_L(0) = 0$ and the initial capacitor voltage $v_C(0) = 0$.


- a Write the elemental, KCL, and KVL equations.
- b Write the second-order differential equation for $v_C(t)$ arranged in the standard form.
- c Convert the initial condition in i_L to a second initial condition in v_C .
- d Let $R = 10 \text{ k}\Omega$, $L = 100 \text{ mH}$, $C = 100 \text{ }\mu\text{F}$, $N = 5$, $A = 5 \text{ V}$, and $\omega = 500 \text{ rad/s}$ and solve for $v_C(t)$.
- e Derive an equation to find $v_o(t)$ from $v_C(t)$. This equation will include derivatives of $v_C(t)$. You don't need to add your solution to part d into this equation.



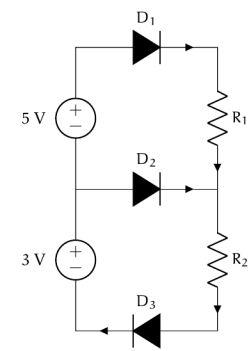Problem unrectangularization


Use the circuit diagram below to answer the following questions. Assume $R_1 = R_2$ and that all diodes are ideal.

- a What state is each diode in?
- b What is the voltage drop across each of the resistors?



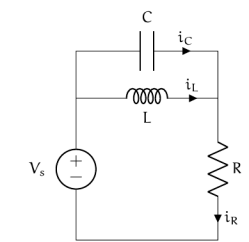
Problem transmittationism

For the circuit diagram below, perform a circuit analysis to solve for the steady state voltage across the resistor R , $v_R(t)$. Assume $V_s = A e^{j\omega t}$ in sine phasor form and $A \in \mathbb{R}$. Express your answer in sine phasor form.



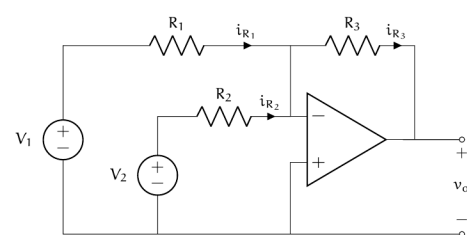Problem kirfunkle

Consider the circuit below with two constant voltage sources V_1 and V_2 . Find the steady state voltage output v_o , assuming $R_1 = R_2 = R_3$. Hint: start solving with the equation $v_o = -v_{R_3}$.



$$R. \frac{d^2 v_C}{dt^2} + \frac{R}{L} \frac{dv_C}{dt} + \frac{1}{LC} v_C = \frac{1}{LC} A \sin(\omega t)$$

$$\frac{d^2 v_C}{dt^2} + 4 \times 10^3 \frac{dv_C}{dt} + 10^5 v_C = 5 \times 10^5 \sin(500t)$$

$$\lambda^2 + 4 \times 10^3 \lambda + 10^5 = 0$$

$$\lambda = \frac{-4 \times 10^3 \pm \sqrt{(4 \times 10^3)^2 - 4(10^5)}}{2}$$

$$\lambda = -25, -3975$$

$$v_{C,p}(t) = C_1 e^{-25t} + C_2 e^{-3975t}$$

$$v_{C,h}(t) = K_1 \sin(500t) + K_2 \cos(500t)$$

$$\frac{dv_{C,h}}{dt} = 500 K_1 \cos(500t) - 500 K_2 \sin(500t)$$

$$\frac{d^2 v_{C,h}}{dt^2} = -25 \times 10^4 K_1 \sin(500t) - 25 \times 10^4 K_2 \cos(500t)$$

$$-25 \times 10^4 K_1 + 2 \times 10^6 K_1 + 10^5 K_2 = 0$$

$$-25 \times 10^4 K_1 - 2 \times 10^6 K_2 + 10^5 K_2 = 5 \times 10^5$$

$$K_1 = -0.0136 \quad K_2 = -0.249$$

$$v_{C,h}(t) = -0.0136 \sin(500t) - 0.249 \cos(500t)$$

$$v_C(t) = v_{C,p}(t) + v_{C,h}(t)$$

$$= C_1 e^{-25t} + C_2 e^{-3975t} - 0.0136 \sin(500t) - 0.249 \cos(500t)$$

$$v_C(0) = 0 \quad \left. \frac{dv_C}{dt} \right|_{t=0} = 0$$

$$\frac{dv_C}{dt} = -25 C_1 e^{-25t} - 3975 C_2 e^{-3975t} - 9.3263 \cos(500t) + 125 \sin(500t)$$

$$-25 C_1 - 3975 C_2 - 9.32 = 0$$

$$C_1 + C_2 - 0.249 = 0$$

$$C_1 = 0.253 \quad C_2 = -0.0039$$

$$v_C(t) = 0.253 e^{-25t} - 0.0039 e^{-3975t} - 0.0136 \sin(500t) - 0.249 \cos(500t)$$