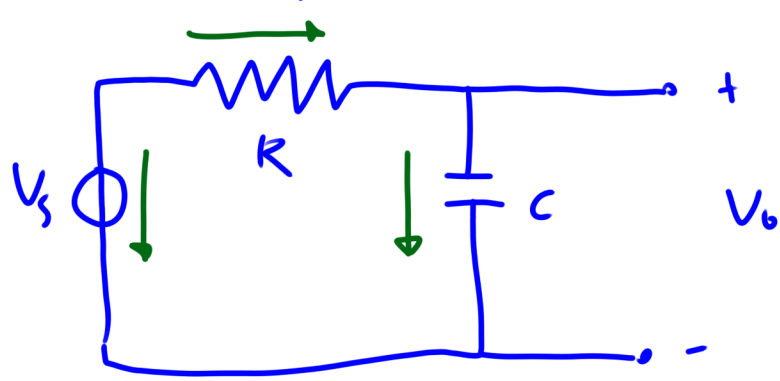


State Space Representation to IO ODE



Solve for V_o

1. Derive ODE directly

2. Linear Graph
Normal Tree
SS Model

Transfer function
ODE

1. Elemental eqns

$$\frac{dv_c}{dt} = \frac{1}{C} i_c = \frac{1}{C} i_R = \frac{1}{RC} V_R$$


$$V_R = R i_R = \frac{V_s - V_c}{RC}$$

KCL $i_R = i_c$

KVL $V_s = V_R + V_c \Rightarrow V_R = V_s - V_c$

$$\frac{dv_c}{dt} + \frac{1}{RC} V_c = \frac{1}{RC} V_s$$

2.

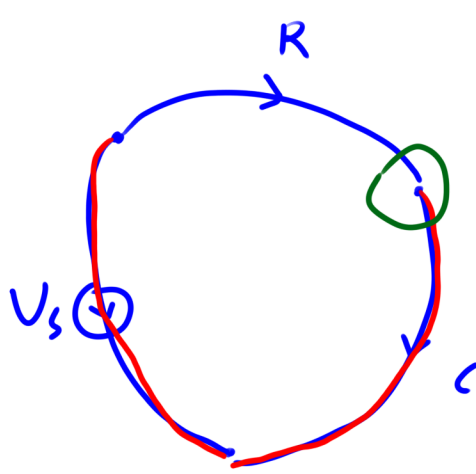

Primary: V_s V_c i_R

Secondary: I_s i_c V_R

state: V_c

$$x = [V_c]$$

$$u = [V_s]$$

$$y = [V_c]$$

Elemental

$$\frac{dv_c}{dt} = \frac{1}{C} i_c = \frac{1}{C} i_R = \frac{V_s - V_c}{RC}$$

$$i_R = \frac{1}{R} V_R = \frac{V_s - V_c}{R}$$

Continuity

$$i_c = i_R$$

compatibility

$$V_R = V_s - V_c$$

$$\dot{x} = Ax + Bu$$

$$\dot{x} = \left[-\frac{1}{RC} \right] x + \left[\frac{1}{RC} \right] u$$

$$y = \underbrace{[1]}_C x + \underbrace{[0]}_D u$$

$$H(s) = (sI - A)^{-1} B + D$$

$$= 1 \left(s(1) - \frac{-1}{RC} \right)^{-1} \frac{1}{RC} + 0$$

$$= \left(s + \frac{1}{RC} \right)^{-1} \frac{1}{RC}$$

$$= \frac{1}{s + \frac{1}{RC}} \frac{1}{RC} = \frac{1}{sRC + 1}$$

$$\frac{RC \frac{dv_c}{dt} + V_c}{RC} = \frac{V_s}{RC}$$

$$\frac{dv_c}{dt} + \frac{1}{RC} V_c = \frac{1}{RC} V_s \quad \checkmark$$

$$\frac{\frac{1}{RC}}{s + \frac{1}{RC}}$$

$$\frac{dv_c}{dt} + \frac{1}{RC} V_c = \frac{1}{RC} V_s$$