

imp.eqiv Norton and Thévenin theorems

1 The following remarkable theorem has been proven.⁵

Theorem imp.1: generalized Thévenin's theorem

Given a linear network of across-variable sources, through-variable sources, and impedances, the behavior at the network's output nodes can be reproduced exactly by a single across-variable source V_e in series with an impedance Z_e .

2 The equivalent linear network has two quantities to determine: V_e and Z_e .

Determining Z_e

3 The equivalent impedance Z_e of a network is the impedance between the output nodes with all inputs set to zero. Setting an across-variable source to zero means the across-variable on both its terminals are equal, which is equivalent to treating them as the same node. Setting a through-variable source to zero means the through-variable through it is zero, which is equivalent to treating its nodes as disconnected.

Determining V_e

4 The equivalent across-variable source V_e is the across-variable at the output nodes of the network when they are left open (disconnected from a load). Determining this value typically requires some analysis with the elemental, continuity, and compatibility equations (preferably via impedance methods).

Norton's theorem

5 Similarly, the following remarkable theorem has been proven.

Theorem imp.2: generalized Norton's theorem

Given a linear network of across-variable sources, through-variable sources, and impedances, the behavior at the network's output nodes can be reproduced exactly by a single through-variable source F_e in parallel with an impedance Z_e .

6 The equivalent network has two quantities to determine: F_e and Z_e . The equivalent impedance Z_e is identical to that of Thévenin's theorem, which leaves the equivalent through-variable source F_e to be determined.

Determining F_e

7 The equivalent through-variable source F_e is the through-variable through the output terminals of the network when they are shorted (collapsed to a single node). Determining this value typically requires some analysis with elemental, continuity, and compatibility equations (preferably via impedance methods).


Converting between Thévenin and Norton equivalents

8 There is an equivalence between the two equivalent network models that allows one to convert from one to another with ease. The equivalent impedance Z_e is identical in each and provides the following equation for converting between the two representations:

Equation 1 converting between Thévenin and Norton equivalents


$$V_e = Z_e F_e$$

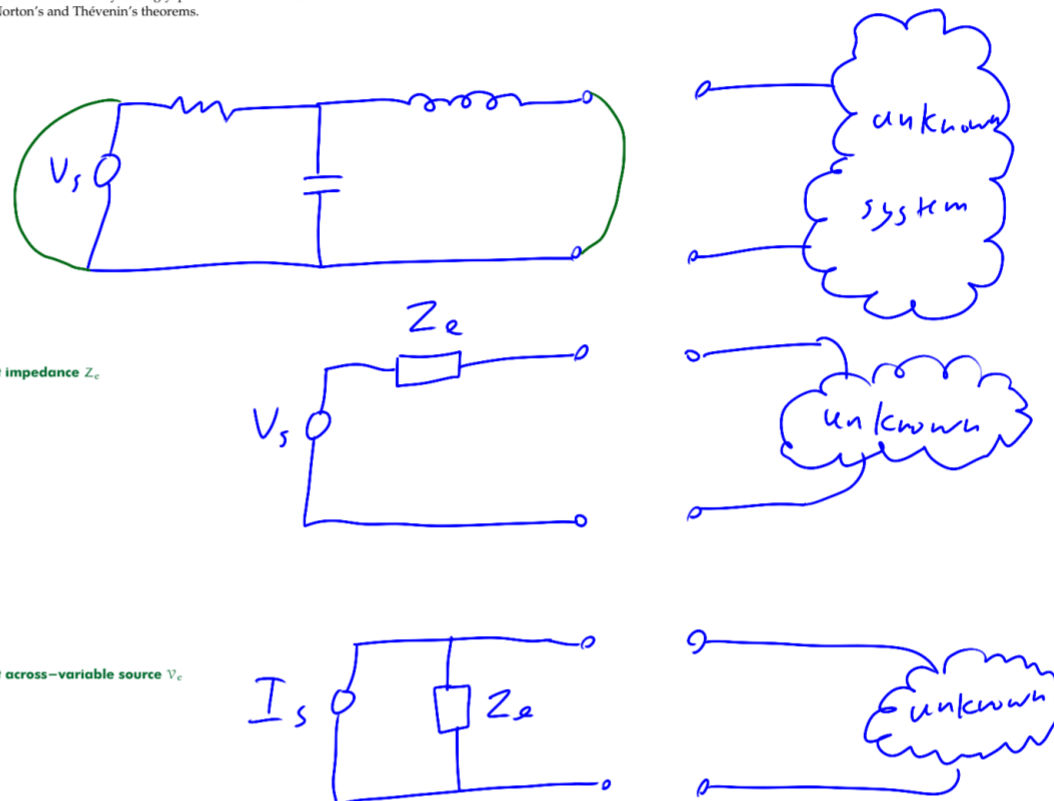5. This lecture is intentionally strongly paralleled in our Electronics lecture on Norton's and Thévenin's theorems.



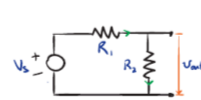Example imp.eqiv-1

For the circuit shown, find a Thévenin and a Norton equivalent.





re: Thévenin and Norton equivalents

$$Z_e = \frac{R_1 R_2}{R_1 + R_2}$$

$$V_e = \frac{R_2}{R_1 + R_2} V_s$$

$$I_e = \frac{V_s}{R_1}$$

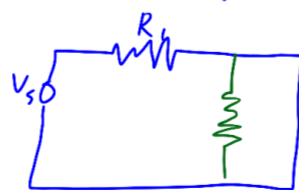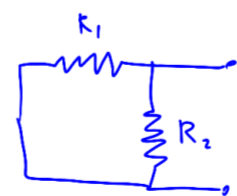

$$V_s = R_1 I_e$$

$$I_e = \frac{V_s}{R_1}$$

$$I_e Z_e = \frac{V_s}{R_1} \frac{R_1 R_2}{R_1 + R_2} = V_s \frac{R_2}{R_1 + R_2} \quad \checkmark$$