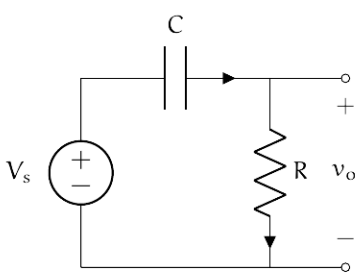


Problem quantizer

Given the circuit below, find the steady state output voltage  $v_o$  in trigonometric form,  $v_o = B \cos(\omega t + \phi)$ , with the input voltage,  $V_s = A \cos(\omega t + \frac{\pi}{4})$ . For this problem:

- a find the output amplitude B, and
- b determine the output phase  $\phi$ .



\_\_\_\_\_/30 p.

$$Z_R = R$$

$$Z_C = \frac{1}{j\omega C}$$

$$V_o = V_s \frac{Z_R}{Z_C + Z_R} = V_s Z$$

$$Z = \frac{R}{\frac{1}{j\omega C} + R} = \frac{j\omega RC}{1 + j\omega RC} \frac{(1 - j\omega RC)}{(1 - j\omega RC)}$$

$$= \frac{j\omega RC + \omega^2 R^2 C^2}{1 + \omega^2 R^2 C^2}$$


$$|Z| = \frac{\sqrt{\omega^2 R^2 C^2 + \omega^2 R^2 C^2}}{1 + \omega^2 R^2 C^2}$$

Problem levitation

In the linear graph and normal tree below a system is depicted consisting of a motor driven by a voltage source  $V_s$  with inertia  $J$  driving a rotary damper and spring connected in series. Let the motor constant be  $K_a$ , and outputs of the system be the rotational velocity of the inertia,  $\Omega_J$ , and the change in rotational velocity across the rotational damper,  $\Omega_B$ .

Given this linear graph and normal tree:

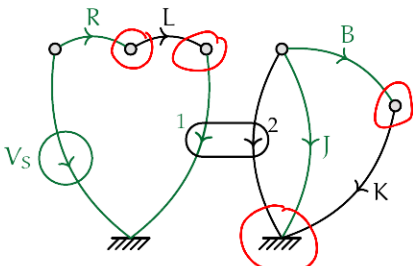- ✓ a determine the state variables,
- ✓ b define the state, input, and output vectors,
- ✓ c write the elemental, continuity, and compatibility equations, and
- d solve for the state and output equations.



\_\_\_\_\_/40 p.

$$\angle(Z) = \tan^{-1}\left(\frac{\omega RC}{\omega^2 R^2 C^2}\right)$$

$$= \tan^{-1}\left(\frac{1}{\omega RC}\right)$$

$$Z = |Z| e^{\angle(Z)}$$

$$V_s = A \cos(\omega t + \frac{\pi}{4}) = A e^{j(\omega t + \frac{\pi}{4})}$$

$$V_o = V_s Z = A e^{j(\omega t + \frac{\pi}{4})} |Z| e^{\angle(Z)}$$

$$= A |Z| e^{j(\omega t + \frac{\pi}{4} + \angle(Z))}$$

$$= A |Z| \cos(\omega t + \frac{\pi}{4} + \angle(Z))$$

$$B = A |Z|$$

$$B = A \frac{\omega RC \sqrt{\omega^2 R^2 C^2 + 1}}{1 + \omega^2 R^2 C^2}$$

$$\phi = \frac{\pi}{4} + \angle(Z)$$

$$\phi = \frac{\pi}{4} + \tan^{-1}\left(\frac{1}{\omega RC}\right)$$

State  $\Omega_J$   $i_L$   $\tau_K$

$$X = \begin{bmatrix} i_L \\ \Omega_J \\ \tau_K \end{bmatrix} \quad U = [V_s] \quad Y = \begin{bmatrix} \Omega_J \\ \Omega_B \end{bmatrix}$$

Primary:  $V_R$   $V_L$   $V_s$   $i_L$   $\Omega_J$   $\Omega_B$   $\tau_K$   $\tau_2$

Elemental:

$$V_R = R i_R = R i_L$$

$$\frac{d i_L}{dt} = \frac{1}{L} V_L = \frac{1}{L} (V_s - V_R - V_L) = \frac{1}{L} (V_s - R i_L - K_a \Omega_J)$$

$$\begin{bmatrix} V_1 \\ i_1 \end{bmatrix} = \begin{bmatrix} \Omega_2 \\ \tau_2 \end{bmatrix} \begin{bmatrix} K_a & 0 \\ 0 & -1/K_a \end{bmatrix} \quad V_1 = \Omega_2 K_a = K_a \Omega_J$$

$$\tau_2 = -K_a i_1 = -K_a i_L$$

$$\frac{d \Omega_J}{dt} = \frac{1}{J} \tau_J = \frac{1}{J} (-\tau_2 - \tau_K) = \frac{1}{J} (K_a i_L - K(\Omega_J - \Omega_B))$$

$$\Omega_B = \frac{1}{B} \tau_B = \frac{1}{B} \tau_K \quad = \frac{1}{J} (K_a i_L - K(\Omega_J - \frac{1}{B} \tau_K))$$

$$\frac{d \tau_K}{dt} = K \Omega_K = K(\Omega_J - \Omega_B) = K(\Omega_J - \frac{1}{B} \tau_K)$$

Continuity:

$$i_R = i_L$$

$$i_1 = i_L$$

$$\tau_B = \tau_K$$

$$\tau_J = -\tau_2 - \tau_K$$

Compatibility:

$$V_L = V_s - V_R - V_1$$

$$\Omega_2 = \Omega_J$$

$$\Omega_K = \Omega_J - \Omega_B$$

$$\dot{X} = \begin{bmatrix} \frac{d i_L}{dt} \\ \frac{d \Omega_J}{dt} \\ \frac{d \tau_K}{dt} \end{bmatrix}$$

$$\dot{X} = \underbrace{\begin{bmatrix} -R/L & -K_a/L & 0 \\ K_a/J & -K/J & K/JB \\ 0 & K & -K/B \end{bmatrix}}_A X + \underbrace{\begin{bmatrix} 1/L \\ 0 \\ 0 \end{bmatrix}}_B U \quad [V_s]$$

$$Y = \begin{bmatrix} \Omega_J \\ \Omega_B \end{bmatrix} = \underbrace{\begin{bmatrix} 0 & 1 & 0 \\ 0 & 0 & 1/B \end{bmatrix}}_C \underbrace{\begin{bmatrix} i_L \\ \Omega_J \\ \tau_K \end{bmatrix}}_X + \underbrace{\begin{bmatrix} 0 \\ 0 \end{bmatrix}}_D [V_s]$$