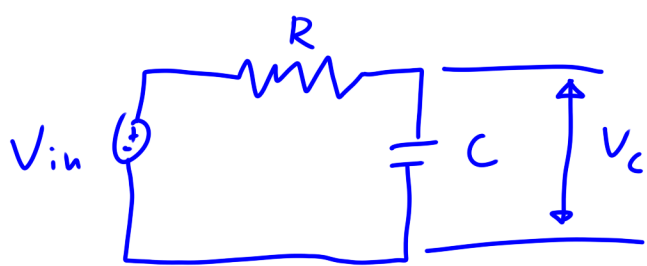
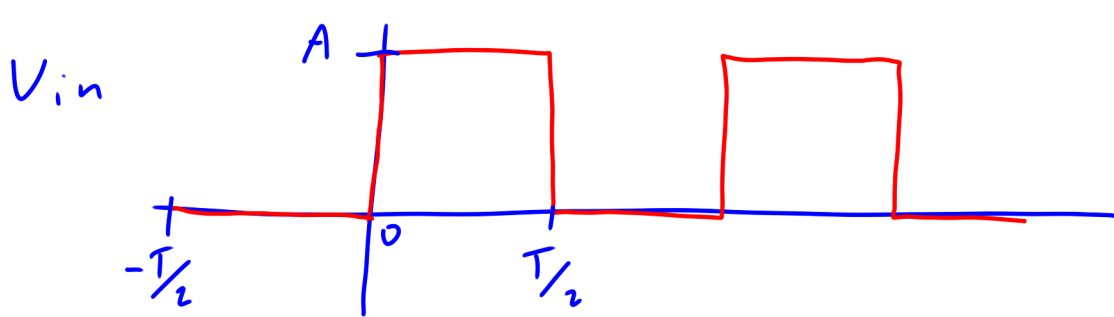


Given an RC circuit with a periodic input, find the voltage across the capacitor



$$H(s) = \frac{1}{1+RCs} = \frac{V_C(s)}{V_{in}(s)}$$



$$a_n = \frac{2}{T} \int_{-T/2}^{T/2} V_{in}(t) \cos(\omega_n t) dt = \frac{2}{T} \int_0^{T/2} A \cos(\omega_n t) dt$$

$$= \frac{2A}{T\omega_n} \sin(\omega_n t) \Big|_0^{T/2} = \frac{2A}{T\omega_n} \sin(\omega_n \frac{T}{2})$$

$$\omega_n = \frac{2\pi n}{T} \quad = \frac{2A}{T\omega_n} \sin\left(\frac{2\pi n}{T} \frac{T}{2}\right) = 0$$

$$a_0 = \frac{2}{T} \int_{-T/2}^{T/2} V_{in}(t) dt = \frac{2}{T} \int_0^{T/2} A dt = \frac{2A}{T} t \Big|_0^{T/2} = \frac{2A}{T} \frac{T}{2} = A$$

$$b_n = \frac{2}{T} \int_{-T/2}^{T/2} V_{in}(t) \sin(\omega_n t) dt = \frac{2}{T} \int_0^{T/2} A \sin(\omega_n t) dt$$

$$= \frac{-2A}{T\omega_n} \cos(\omega_n t) \Big|_0^{T/2} = \frac{-2A}{T\omega_n} \cos(\omega_n \frac{T}{2}) + \frac{2A}{T\omega_n}$$

$$= \frac{2A}{T\omega_n} (1 - \cos(\omega_n \frac{T}{2})) = \frac{2A}{\cancel{2\pi n} \cancel{T}} (1 - \cos(\frac{2\pi n}{\cancel{T}} \frac{\cancel{T}}{2})) = \frac{A}{n\pi} (1 - \cos(n\pi))$$

$$V_{in}(t) = \frac{a_0}{2} + \sum_{n=1}^{\infty} b_n \sin(\omega_n t)$$

$$H(j\omega) = H(s) \Big|_{s \rightarrow j\omega} = \frac{1}{1+RCs} \Big|_{s \rightarrow j\omega} = \frac{1}{1+RCj\omega} \frac{1-RCj\omega}{1-RCj\omega} = \frac{1-RCj\omega}{1+(RC\omega)^2}$$

$$\operatorname{Re}(H(j\omega)) = \frac{1}{1+(RC\omega)^2} \quad \operatorname{Im}(H(j\omega)) = \frac{-RC\omega}{1+(RC\omega)^2}$$

$$|H(j\omega)| = \sqrt{\operatorname{Re}(H(j\omega))^2 + \operatorname{Im}(H(j\omega))^2}$$

$$= \sqrt{\left(\frac{1}{1+(RC\omega)^2}\right)^2 + \left(\frac{-RC\omega}{1+(RC\omega)^2}\right)^2}$$

$$= \frac{\sqrt{1+(RC\omega)^2}}{1+(RC\omega)^2} = \frac{1}{\sqrt{1+(RC\omega)^2}}$$

$$\angle H(j\omega) = \tan^{-1} \left( \frac{\operatorname{Im}(H(j\omega))}{\operatorname{Re}(H(j\omega))} \right) = \tan^{-1} \left( \frac{\frac{-RC\omega}{1+(RC\omega)^2}}{\frac{1}{1+(RC\omega)^2}} \right) = \tan^{-1}(-RC\omega)$$

$$V_C(t) = H(j0) \frac{a_0}{2} + \sum_{n=1}^{\infty} b_n |H(j\omega_n)| \sin(\omega_n t + \angle H(j\omega_n))$$