

imp.ip Input impedance and admittance

1. We now introduce a generalization of the familiar impedance and admittance of electrical circuit analysis, in which system behavior can be expressed algebraically instead of differentially. We begin with generalized input impedance.
2. Consider a system with a source, as shown in Fig. ip.1. The source can be either an across- or a through-variable source. The ideal source specifies either V_{in} or \mathcal{F}_{in} , and the other variable depends on the system.
3. Let a source variables have Laplace transforms $V_{in}(s)$ and $\mathcal{F}_{in}(s)$. We define the system's input impedance Z and input admittance Y to be the Laplace-domain ratios

$$Z(s) = \frac{V_{in}(s)}{\mathcal{F}_{in}(s)} \quad \text{and} \quad Y(s) = \frac{\mathcal{F}_{in}(s)}{V_{in}(s)} \quad (1)$$

Clearly,

$$Y(s) = \frac{1}{Z(s)}$$

Both Z and Y can be considered transfer functions: for a through-variable source \mathcal{F}_{in} , the impedance Z is the transfer function to across-variable V_{in} ; for an across-variable source V_{in} , the admittance Y is the transfer function to through-variable \mathcal{F}_{in} . Often, however, we use the more common impedance Z to characterize systems with either type of source.

4. Note that Z and Y are system properties, not properties of the source. An impedance or

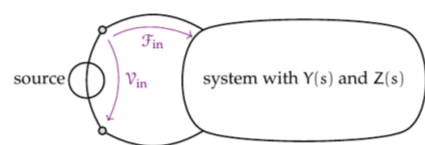


Figure ip.1:

admittance can characterize a system of interconnected elements, or a system of a single element, as the next section explores.

Impedance of ideal passive elements

5. The impedance and admittance of a single, ideal, one-port element is defined from the Laplace transform of its elemental equation.

Generalized capacitors A generalized capacitor has elemental equation

$$\frac{dV_C(t)}{dt} = \frac{1}{C} \mathcal{F}_C(t), \quad (2)$$

the Laplace transform of which is

$$sV_C(s) = \frac{1}{C} \mathcal{F}_C(s), \quad (3)$$

which can be solved for impedance $Z_C = V_C/\mathcal{F}_C$ and admittance $Y_C = \mathcal{F}_C/V_C$:

$$Z_C(s) = \frac{1}{Cs} \quad Y_C(s) = Cs$$

Generalized inductors A generalized inductor has elemental equation

$$\frac{d\mathcal{F}_L(t)}{dt} = \frac{1}{L} V_L(t), \quad (4)$$

the Laplace transform of which is

$$s\mathcal{F}_L(s) = \frac{1}{L} V_L(s), \quad (5)$$

which can be solved for impedance $Z_L = V_L/\mathcal{F}_L$ and admittance $Y_L = \mathcal{F}_L/V_L$:

$$Z_L(s) = Ls \quad Y_L(s) = \frac{1}{Ls}$$

Generalized resistors A generalized resistor has elemental equation

$$V_R(t) = \mathcal{F}_R(t)R, \quad (6)$$

the Laplace transform of which is

$$V_R(s) = \mathcal{F}_R(s)R, \quad (7)$$

which can be solved for impedance $Z_R = V_R/\mathcal{F}_R$ and admittance $Y_R = \mathcal{F}_R/V_R$:

$$Z_R = R \quad Y_R = \frac{1}{R}$$

6. For a summary of the impedance of one-port elements, see Table els.1.

Impedance of interconnected elements

7. As with electrical circuits, impedances of linear graphs of interconnected elements can be combined in two primary ways: in parallel or in series.

8. Elements sharing the same through-variable are said to be in series connection. N elements connected in series $\circ \sum_1 \circ \sum_2 \circ \dots$ have equivalent impedance Z and admittance Y :

$$Z(s) = \sum_{i=1}^N Z_i(s) \quad \text{and} \quad Y(s) = 1 / \sum_{i=1}^N 1/Y_i(s) \quad (8)$$

series

$$N = z$$

$$Y(s) = \frac{1}{\frac{1}{Y_1} + \frac{1}{Y_2}}$$

9. Conversely, elements sharing the same across-variable are said to be in parallel connection. N elements connected in parallel $\leftarrow \sum_1 \rightarrow$ have equivalent impedance Z and admittance Y :


$$Z(s) = 1 / \sum_{i=1}^N 1/Z_i(s) \quad \text{and} \quad Y(s) = \sum_{i=1}^N Y_i(s). \quad (9)$$

parallel

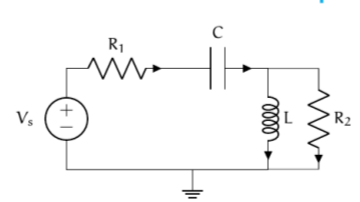Example imp.ip-1

re: input impedance of a simple circuit

For the circuit shown, find the input impedance.



$$Y_{LR_2} = Y_L + Y_{R_2} \quad Z_{LR_2} = \frac{1}{Y_L + Y_{R_2}} = \frac{1}{\frac{1}{Z_L} + \frac{1}{Z_{R_2}}}$$

$$Z = Z_{R_1} + Z_C + Z_{LR_2}$$

$$= Z_{R_1} + Z_C + \frac{Z_{R_1} Z_L}{Z_{R_1} + Z_L}$$