

## imp.eqiv Norton and Thévenin theorems

1 The following remarkable theorem has been proven.<sup>5</sup>

**Theorem imp.1: generalized Thévenin's theorem**

Given a linear network of across-variable sources, through-variable sources, and impedances, the behavior at the network's output nodes can be reproduced exactly by a single across-variable source  $V_e$  in series with an impedance  $Z_e$ .

2 The equivalent linear network has two quantities to determine:  $V_e$  and  $Z_e$ .

Determining  $Z_e$

3 The equivalent impedance  $Z_e$  of a network is the impedance between the output nodes with all inputs set to zero. Setting an across-variable source to zero means the across-variable on both its terminals are equal, which is equivalent to treating them as the same node. Setting a through-variable source to zero means the through-variable through it is zero, which is equivalent to treating its nodes as disconnected.

Determining  $V_e$

4 The equivalent across-variable source  $V_e$  is the across-variable at the output nodes of the network when they are left open (disconnected from a load). Determining this value typically requires some analysis with the elemental, continuity, and compatibility equations (preferably via impedance methods).

Norton's theorem

5 Similarly, the following remarkable theorem has been proven.

**Theorem imp.2: generalized Norton's theorem**

Given a linear network of across-variable sources, through-variable sources, and impedances, the behavior at the network's output nodes can be reproduced exactly by a single through-variable source  $\mathcal{F}_e$  in parallel with an impedance  $Z_e$ .

6 The equivalent network has two quantities to determine:  $\mathcal{F}_e$  and  $Z_e$ . The equivalent impedance  $Z_e$  is identical to that of Thévenin's theorem, which leaves the equivalent through-variable source  $\mathcal{F}_e$  to be determined.

Determining  $\mathcal{F}_e$

7 The equivalent through-variable source  $\mathcal{F}_e$  is the through-variable through the output terminals of the network when they are shorted (collapsed to a single node). Determining this value typically requires some analysis with elemental, continuity, and compatibility equations (preferably via impedance methods).

Converting between Thévenin and Norton equivalents


8 There is an equivalence between the two equivalent network models that allows one to convert from one to another with ease. The equivalent impedance  $Z_e$  is identical in each and provides the following equation for converting between the two representations:

**Equation 1 converting between Thévenin and Norton equivalents**


$$V_e = Z_e \mathcal{F}_e$$
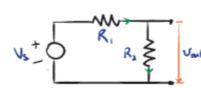
### Example imp.eqiv-1

For the circuit shown, find a Thévenin and a Norton equivalent.


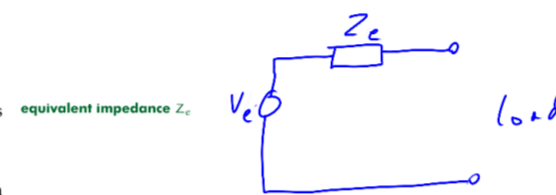
<sup>5</sup> This lecture is intentionally strongly paralleled in our Electronics lecture on Norton's and Thévenin's theorems.



equivalent across-variable source  $V_e$

equivalent through-variable source  $\mathcal{F}_e$

re: Thévenin and Norton equivalents