

## imp.eqiv Norton and Thévenin theorems

1 The following remarkable theorem has been proven.<sup>5</sup>

**Theorem imp.1: generalized Thévenin's theorem**


Given a linear network of across-variable sources, through-variable sources, and impedances, the behavior at the network's output nodes can be reproduced exactly by a single across-variable source  $V_e$  in series with an impedance  $Z_e$ .



2 The equivalent linear network has two quantities to determine:  $V_e$  and  $Z_e$ .

Determining  $Z_e$

3 The equivalent impedance  $Z_e$  of a network is the impedance between the output nodes with all inputs set to zero. Setting an across-variable source to zero means the across-variable on both its terminals are equal, which is equivalent to treating them as the same node. Setting a through-variable source to zero means the through-variable through it is zero, which is equivalent to treating its nodes as disconnected.

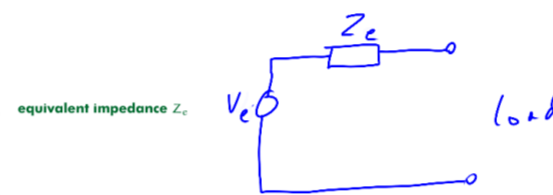

Determining  $V_e$

4 The equivalent across-variable source  $V_e$  is the across-variable at the output nodes of the network when they are left open (disconnected from a load). Determining this value typically requires some analysis with the elemental, continuity, and compatibility equations (preferably via impedance methods).



**Norton's theorem**

5 Similarly, the following remarkable theorem has been proven.

**Theorem imp.2: generalized Norton's theorem**

Given a linear network of across-variable sources, through-variable sources, and impedances, the behavior at the network's output nodes can be reproduced exactly by a single through-variable source  $\mathcal{F}_e$  in parallel with an impedance  $Z_e$ .

6 The equivalent network has two quantities to determine:  $\mathcal{F}_e$  and  $Z_e$ . The equivalent impedance  $Z_e$  is identical to that of Thévenin's theorem, which leaves the equivalent through-variable source  $\mathcal{F}_e$  to be determined.

Determining  $\mathcal{F}_e$

7 The equivalent through-variable source  $\mathcal{F}_e$  is the through-variable through the output terminals of the network when they are shorted (collapsed to a single node). Determining this value typically requires some analysis with elemental, continuity, and compatibility equations (preferably via impedance methods).

**equivalent through-variable source  $\mathcal{F}_e$**

**Converting between Thévenin and Norton equivalents**


8 There is an equivalence between the two equivalent network models that allows one to convert from one to another with ease. The equivalent impedance  $Z_e$  is identical in each and provides the following equation for converting between the two representations:

**Equation 1 converting between Thévenin and Norton equivalents**


$$V_e = Z_e \mathcal{F}_e$$

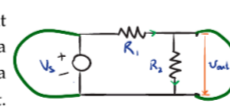**Example imp.eqiv-1**

For the circuit shown, find a Thévenin and a Norton equivalent.



re: Thévenin and Norton equivalents

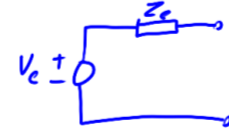

$$Z_e = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2}} = \frac{R_1 R_2}{R_1 + R_2}$$

$$V_e = \frac{R_2}{R_1 + R_2} V_s$$

$$I_e = \frac{V_s}{R_1}$$

$$\mathcal{F}_e Z_e = V$$

$$V_e = I_e Z_e$$

$$\begin{aligned} \frac{R_2}{R_1 + R_2} V_s &= \frac{V_s}{R_1} \frac{R_1 R_2}{R_1 + R_2} \\ &= \frac{R_2}{R_1 + R_2} V_s \quad \checkmark \end{aligned}$$