
05.4 Debouncing circuits for switches

When a mechanical switch is thrown via a button, toggle, or some other interface, the new contact between the two conductors is not immediately seamless. In fact, over a few milliseconds, contact is made and broken dozens of times². This phenomenon is called switch contact bounce.

Often, we mitigate switch bounce with a circuit—called a debouncing circuit—between the switch and the microcontroller. Debouncing circuits yield a single transition of the digital signal, low-to-high or high-to-low.

Consider in detail the debouncing circuit of Fig. 05.1. For the outputs to switch, both inputs must switch, effectively mitigating bounce.

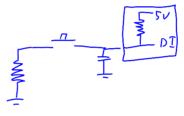



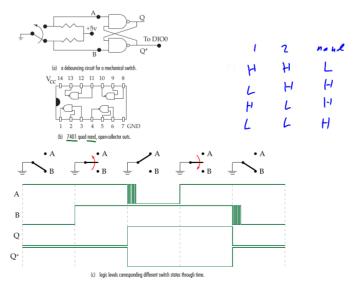


Figure 05.1: an illustration of the operation of a debouncing circuit. With the switch initially drawing B low, Ω^* must be high and Ω low. The loss of contact with B does not affect Ω^* or Ω . Initial contact with A draws a low and therefore Ω high and Ω^* low. The ensuing bounce doesn't affect Ω because it doesn't affect Ω^* being low, so Ω is high, regardless of Λ . This log is then mintrored in the transition from contact with A to B, with its ensuing bounce. A TTL IC, shown in (b), can be used to instantiate this circuit.