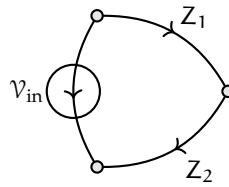


## imp.divide The divider method

1 In Electronics, we developed the useful voltage divider formula for quickly analyzing how voltage divides among series electronic impedances. This can be considered a special case of a more general across-variable divider equation for any elements described by an impedance. After developing the across-variable divider, we also introduce the through-variable divider, which divides an input through-variable among parallel elements.



**Figure divide.1:** the two-element across-variable divider.

**across-variable divider**

### Across-variable dividers

2 First, we develop the solution for the two-element across-variable divider shown in [Figure divide.1](#). We choose the across-variable across  $Z_2$  as the output. The analysis follows the impedance method of [Lecture imp.tf](#), solving for  $v_2$ .

1. Derive four independent equations.
  - a) The normal tree is chosen to consist of  $v_{in}$  and  $Z_2$ .
  - b) The elemental equations are
  - c) The continuity equation is
  - d) The compatibility equation is

2. Solve for the output  $v_2$ . From the elemental equation for  $Z_2$ ,

$$\begin{aligned}
 v_2 &= \mathcal{F}_\infty Z_2 \\
 &= \frac{v_1}{Z_1} Z_2 \\
 &= \frac{Z_2}{Z_1} (v_{\text{in}} - v_2) \quad \Rightarrow \\
 v_2 &= \frac{Z_2}{Z_1 + Z_2} v_{\text{in}}.
 \end{aligned}$$

3 A similar analysis can be conducted for  $n$  impedance elements.

**Equation 1 general across-variable divider**

Through-variable dividers

4 By a similar process, we can analyze a network that divides a through-variable into  $n$  parallel impedance elements.

**Equation 2 general through-variable divider**

Transfer functions using dividers

5 An excellent shortcut to deriving a transfer function is to use the across- and through-variable divider rules instead of solving the system of algebraic equations, as in [Lec. imp.tf](#). An algorithm for this process is as follows.

1. Identify the element associated with an output variable  $Y_i$ . Call it the output element.
2. Identify the source associated with an input variable  $U_j$ . Set all other sources to zero.
3. Transform the network to be an across- or through-variable divider that includes the “bare” (uncombined) output element’s output variable.<sup>6</sup>
  - a) If necessary, form equivalent impedances of portions of the network, being sure to leave the output element’s output variable alone.
  - b) If necessary, transform the source à la Norton or Thévenin.
4. Apply the across- or through-variable divider equation.
5. If necessary, use the elemental equation of the output element to trade output across- and through-variables.
6. If necessary, use the source transformation equation of the input to trade input across- and through-variables.
7. Divide both sides by the input variable.

6. In other words, if the across-variable of the output element is the output, do not combine it in series; if the through-variable is the output, do not combine it in parallel.

<sup>6</sup> It turns out that, despite its many “if necessary” clauses, very often this “shortcut” is easier than the method of [Lecture imp.tf](#) for low-order systems if only a few transfer functions are of interest.

**Example imp.divide-1****re: a circuit transfer function using a divider**

Given the circuit shown with voltage source  $V_s$  and output  $v_L$ ,

- what is the transfer function  $\frac{V_L}{V_s}$ ?
- Without transforming the source, find the transfer function  $\frac{I_L}{V_s}$ .
- Transforming the source, find  $\frac{I_L}{V_s}$ .

