

nlmul.dio Diodes

Diodes are single-port nonlinear elements that, approximately, conduct current in only one direction. We will consider the ubiquitous semiconductor diode, varieties of which include the light-emitting diode (LED), photodiode (for light sensing), Schottky diode (for fast switching), and Zener diode (for voltage regulation). See Fig. dio.1 for corresponding circuit symbols.

In most cases, we use the diode to conduct current in one direction and block reverse current.⁴ When conducting current in its forward direction, it is said to have forward-bias; when blocking current flow in its reverse direction, it is said to have reverse-bias. If the reverse breakdown voltage is reached, current will flow in the reverse direction. It is important to check that a circuit design does not subject a diode to its breakdown voltage, except in special cases (e.g. when using a Zener diode). We begin with a nonlinear model of the voltage-current v_D - i_D relationship. Let

- I_s be the saturation current (typically $\sim 10^{-12}$ A) and
- $V_{TH} = k_b T/e$ be the thermal voltage (at room temperature ~ 25 mV) with⁵
 - k_b the Boltzmann constant,
 - e the fundamental charge, and
 - T the diode temperature.

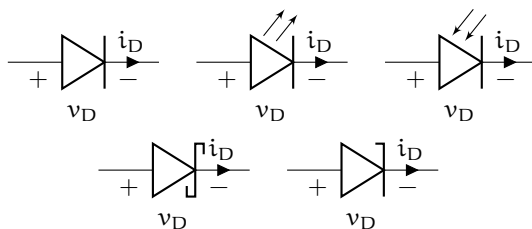


Figure dio.1: diode symbols. From left to right, the generic symbol, LED, photodiode, Schottky, Zener.

semiconductor diode

light-emitting diode (LED)

photodiode

Schottky diode

Zener diode

4. The paradigmatic exception is the Zener diode, which is typically used in reverse bias in order to take advantage of its highly stable reverse bias voltage over a large range of reverse current. We will not consider this application here.

forward-bias

reverse-bias

breakdown voltage

5. Unless otherwise specified, it is usually reasonable to assume room-temperature operation.

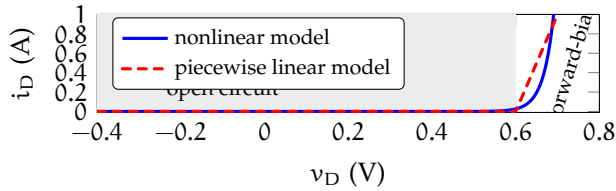



Figure dio.2: the voltage-current relationship in the nonlinear and piecewise linear models. In the figure, $R_d = 0.1 \Omega$.

Equation 1 nonlinear diode model

See Fig. dio.2 for a plot of this function. One can analyze circuits with diodes using the methods of Chapter can and Eq. 1 as the diode’s elemental equation. A nonlinear set of equations results, which typically require numerical solution techniques.

A piecewise linear model

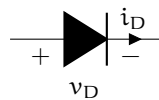An ideal diode is one that is a perfect insulator (open circuit, $i_D = 0$) for $v_D < 0$ conductor for $v_D > 0$. We use the symbol shown in Fig. dio.3 for the ideal diode.




ideal diode

Figure dio.3: circuit symbol for an ideal diode. Note that this is a nonstandard use of this symbol.

At times, the ideal diode is sufficient to model a diode; often, however, we prefer a more accurate model that is piecewise linear.

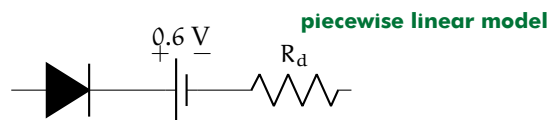The piecewise linear model is shown in Fig. dio.4. It includes an ideal diode in series with a fixed voltage drop of 0.6 V and a resistor with resistance R_d . This approximates the nonlinear model with two linear approximations.



piecewise linear model

Figure dio.4: piecewise linear model.

Equation 2 piecewise linear diode model

See Fig. dio.2 for a plot of this function and a comparison to the nonlinear model.

The slope in forward-bias is $1/R_d$. This model's effectiveness is highly dependant on R_d , so an operating point must be chosen and R_d chosen to match most closely with the nonlinear model near that operating point.

operating point

Method of assumed states

The method of assumed states is a method for using linear circuit analysis to analyze circuits with nonlinear components. The method is summarized in the following steps.

method of assumed states

1. Begin at the initial time $t = 0$.
2. Replace each diode in the circuit diagram with the piecewise linear diode model.
3. Proceed with the circuit analysis of Chapter can, ignoring the elemental equations for the ideal diodes D_i . Your system of equations will have unknown ideal diode current i_{D_i} and voltage v_{D_i} . Simplify it to the extent possible.
4. Guess the current state of each ideal diode: ON or OFF. For each ideal diode D_i guessed to be ON,

$$\text{set } v_{D_i} = 0 \text{ and assume that } i_{D_i} > 0. \quad (3)$$

For each ideal diode assumed to be OFF,

$$\text{set } i_{D_i} = 0 \text{ and assume that } v_{D_i} < 0. \quad (4)$$

For n diodes in the circuit, there are 2^n possibilities at each moment in time.

Guess just one to start.

5. If even one diode violates its assumption from above, dismiss the results and return to step 4 and choose a different combination of assumed states (consider flipping the assumptions on those diodes that violated the old assumptions).
6. If not even one diode violates its assumptions, this is the correct solution for this moment in time.
7. This solution is valid for as long as its assumptions are valid. Once they fail, go back to step 4.


Since impedance methods are valid only for linear circuits, steady-state analyses should proceed with the same process outlined above.

With a periodic input, a periodic (steady) solution may emerge.

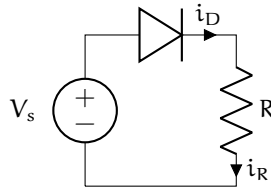Example nlnmul.dio-1

re: half wave rectifier

Given the circuit shown with voltage source $V_s(t) = 3 \cos 2\pi t$, what is the output v_R ? Explain why this might be called a “half-wave rectifier.” Let $R = 10 \Omega$.







An algorithm for determining R_d

The piecewise linear approximation of the exponential diode current will never be great, but we can at least try to choose R_d in a somewhat optimal way, recognizing that when highly accurate results are required, there's no substitute for the nonlinear model.

Consider the algorithm of Fig. dio.6. Initially set

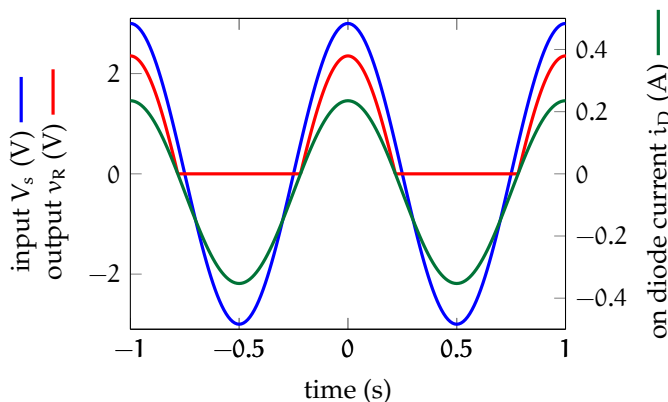


Figure dio.5: the input and output voltage of the half-wave rectifier circuit of Example nlnmul.dio-1. Note that the “on” diode subcircuit is valid for $i_D > 0$ and the “off” diode circuit is valid for $i_D < 0$.

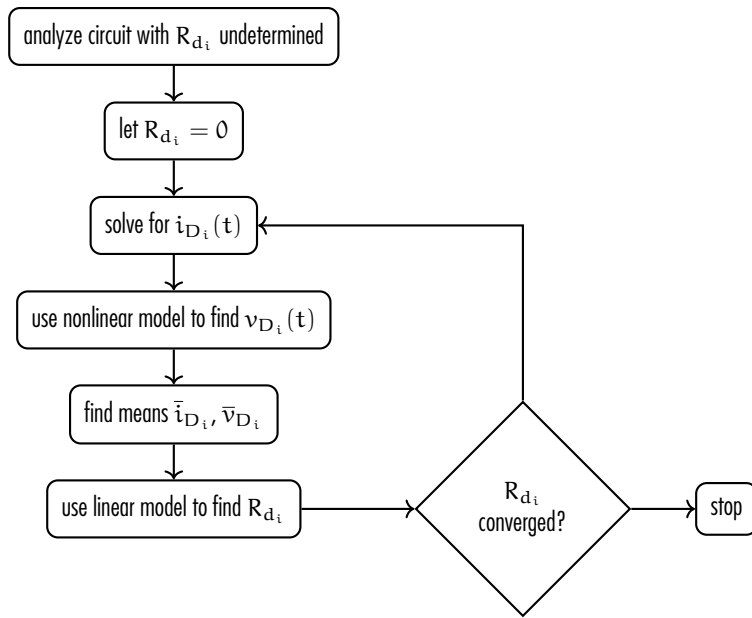


Figure dio.6: an algorithm for determining R_{d_i} .

to zero the diode resistances R_{d_i} of each resistor. Solve for each diode current $i_{D_i}(t)$, then use this to find $v_{D_i}(t)$ from the nonlinear model of Eq. 1:

$$v_{D_i}(t) = V_{TH} \ln(i_{D_i}(t)/I_s + 1). \quad (5)$$

Now take the means of these signals (assuming steady state oscillation) over a period T , excluding the time T_0 during which the diode voltage was in reverse-bias:⁶

$$\bar{i}_{D_i} = \frac{1}{T - T_0} \int_{t_0}^{t_0+T} i_{D_i}(\tau) d\tau \quad (6a)$$

$$\bar{v}_{D_i} = \frac{1}{T - T_0} \int_{t_0}^{t_0+T} v_{D_i}(\tau) d\tau. \quad (6b)$$

Now use the piecewise linear model of ?? to estimate R_{d_i} :

$$R_{d_i} = \frac{\bar{v}_{D_i} - 0.6V}{\bar{i}_{D_i}}. \quad (7)$$

We can use this estimate of R_{d_i} to re-analyze the circuit and repeat the same process of deriving a new estimate of R_{d_i} . This process should converge on an estimate of R_{d_i} that is in some sense optimal.

6. Note that if T_0 is ignored, our estimate of R_d will include the effects of time during which no current is flowing and the diode is in reverse-bias, during which time R_d is not applicable.

Note that if, during this iterative process, one finds $\bar{v}_{D_i} < 0.6 \text{ V}$, a negative R_d will result. At this point, a couple different reasonable approaches can be taken:

1. just use $R_{d_i} = 0$ or
2. use some reasonably central value of $\bar{v}_{D_i} > 0.6 \text{ V}$.

The second case is preferred if $v_{D_i}(t)$ spends much time above 0.6 V . But usually, if it spends much time, the mean \bar{v}_{D_i} should be great enough to avoid this situation. Circuits that tend to express this behavior are those with high impedance and correspondingly low currents.