

nlmul.fet MOSFETs

A metal–oxide–semiconductor field-effect transistor (MOSFET) is a two-port, nonlinear circuit element that lies at the heart of digital electronics, with sometimes millions integrated into a single microprocessor. They are the dominant type of transistor, a class of elements that includes the bipolar junction transistor (BJT).

MOSFETs are not just common in integrated circuits made of silicon, they are also available as discrete elements, which is the form most often encountered by the mechatronicist.

There are two primary types of MOSFET: the n-channel and the p-channel, determined by the type of semiconductor doping (negative or positive) used in the manufacturing process. These types are “opposites,” so we choose to focus on n-channel, here.

Fig. fet.1 displays the circuit diagram symbol for the MOSFET. There are three⁷ terminals: the gate G, drain D, and source S. The current

flowing from one terminal to another is labeled with consecutive subscripts; for instance, the current flowing from drain to source is i_{DS} . Similarly, the voltage drop across two terminals is labeled with concurrent subscripts; for instance, the voltage drop from gate to source is v_{GS} .

The input-output characteristics of the MOSFET are quite complex, but we may, in the first approximation, consider it to be like a switch. In this model, called the S-model, if the gate voltage v_{GS} is less than the threshold voltage V_T (typically around 0.7 V), the D and S terminals are disconnected (open) from each other (OFF mode). But when $v_{GS} > V_T$, D and S are connected via a short and current i_{DS} can flow

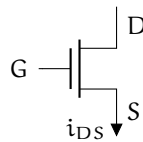


Figure fet.1: circuit symbol for a n-channel MOSFET.

transistor

bipolar junction transistor (BJT)

n-channel MOSFET

p-channel MOSFET

7. Note that if we consider the gate-side to be the input with $i_{GS} = 0$ and v_{GS} and the drain-source-side to be the output with i_{DS} and v_{DS} , the MOSFET can be seen to be two-port.

gate G

drain D

source S

switch S-model

threshold voltage

(ON mode).

The input-output characteristics of a MOSFET are actually much more complex than the S-model captures. The S-model can build intuition and suffice for digital logic circuit analysis. However, we are here mostly concerned with analog circuit models. Specifically, we mechatronicists use MOSFETs to drive power-hungry loads (e.g. motors) with high-power sources controlled by low-power microcontrollers. We now turn to a general model, after which we consider a method of analyzing MOSFET circuits.

The switch unified (SU) model

The switch unified (SU) model is reasonably accurate at describing actual MOSFET input-output characteristics. However, it is quite nonlinear, and therefore can give us headaches during analysis. As usual, we are concerned with the element's voltage-current relationships.

switch unified (SU) model

Definition nlnmul.2: switch unified model

Let K be a constant parameter of the MOSFET with units A/V^2 . K can be found from parameters of a given MOSFET. The current into the gate is zero: $i_G = 0$. The current from drain to source is controlled by the two voltage variables v_{GS} and v_{DS} , as shown.

$$i_{DS} = \begin{cases} 0 & \text{for } v_{GS} < V_T \\ K((v_{GS} - V_T)v_{DS} - v_{DS}^2/2) & \text{for } v_{GS} \geq V_T \text{ and } v_{DS} < v_{GS} - V_T \\ \frac{K}{2}(v_{GS} - V_T)^2 & \text{for } v_{GS} \geq V_T \text{ and } v_{DS} \geq v_{GS} - V_T \end{cases}$$

So, as in the S-model, the gate voltage v_{GS} must exceed the threshold voltage V_T for current to flow. The interval below the threshold is called the cutoff region (OFF). Note, however, that current doesn't just flow freely, as it would with the short of the S-model. In fact, two distinct

cutoff region

ON ($v_{GS} > V_T$) intervals emerge. In both, the current i_{DS} depends on v_{GS} . In the triode region, $v_{DS} < v_{GS} - V_T$, i_{DS} also depends on v_{DS} . However, in the saturation region, $v_{DS} > v_{GS} - V_T$, i_{DS} is independent of v_{DS} and can be controlled by v_{GS} , alone.

Note that in saturation, the MOSFET behaves like a current source controlled by v_{GS} . A source controlled by a variable in the circuit is called a dependent source. This behavior as a dependent current source (that can also be turned off) is the most valuable for us.

The switch current source (SCS) model is actually just a recognition of this behavior and an elimination of the triode region from consideration. This is a reasonable assumption if we can guarantee operation in cutoff or saturation only.

Given the piecewise MOSFET models, we can again use the method of assumed states for MOSFET circuit analysis. Note however that only the S-model is piecewise linear and that the SU- and SCS-models are piecewise nonlinear. We can handle some relatively simple nonlinear cases analytically, but require either linearization or numerical assistance for more complex circuit analyses.

triode region

saturation region


dependent source

switch current source (SCS) model

method of assumed states

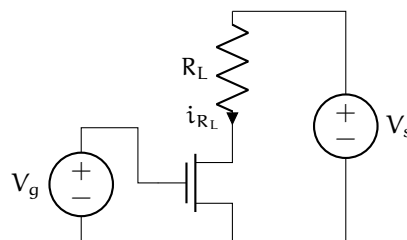Example nlnmul.fet-1

Given the circuit shown, solve for the voltage across the load R_L for varying V_g given the following conditions: saturation of the MOSFET, $R_L = 1 \text{ k}\Omega$, $K = 0.5 \text{ mA/V}^2$, $V_T = 0.7 \text{ V}$, $V_s = 10 \text{ V}$.



re: transformers and impedance



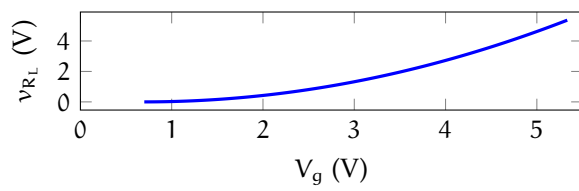


Figure fet.2: the load voltage as a function of gate voltage for Example nlnmul.fet-1.